


S.E. Sem. III [CMPN]
Digital Logic Design and Analysis
 Prelim Question Paper Solution

Time : 3 Hrs.]

[Marks : 80

Q.1(a) Implement Ex-OR gate using Four NAND gates only. [5]


(A)

 

$$\begin{aligned} (A \cdot AB)(B \cdot AB) &= A \cdot AB + B \cdot AB &= A(\bar{A} + \bar{B}) + B(\bar{A} + \bar{B}) \\ &= A\bar{A} + A\bar{B} + \bar{A}B + B\bar{B} &= \bar{A}B + A\bar{B} &= A \oplus B \end{aligned}$$

Q.1(b) Explain TTL NAND gate. [5]

(A) Circuit diagram :

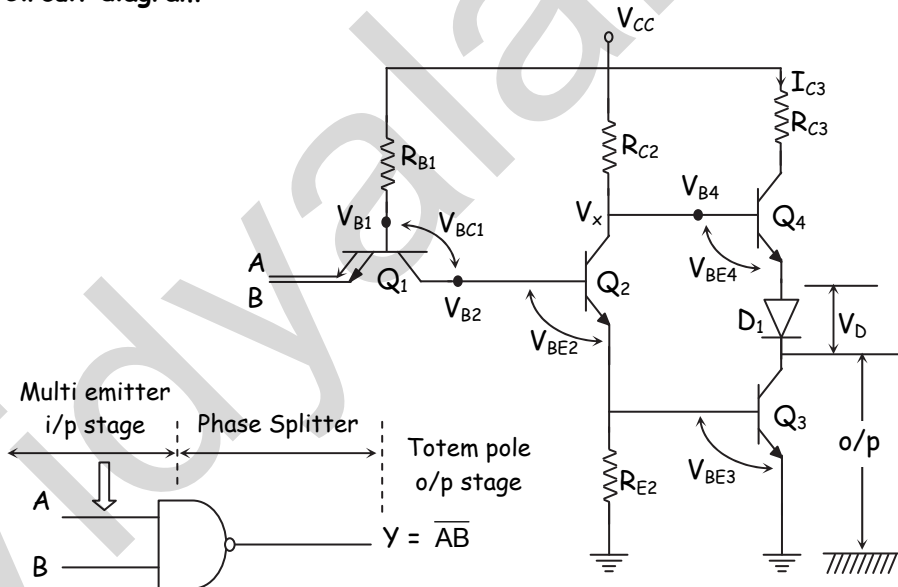

A	B	Y = \overline{AB}
0	0	1
0	1	1
1	0	1
1	1	0

Operation :

Case I : $A = 0, B = 0$

For this case Q_1 works in normal mode and transistors Q_2 and Q_3 both will be OFF and voltage at V_x point will be V_{CC} and this is sufficient to turn ON Q_4 and D_1 (because to turn ON Q_4 and D_1 voltage $V_x = V_{B4} = V_{BE4} + V_{D1} = 0.7 + 0.7 = 1.4$ V) so Q_4 and D_1 both will be ON when output V_0 .

$$\begin{aligned} V_0 &= V_x - V_{BE4} - V_{D1} \\ &= V_{CC} - V_{BE4} - V_{D1} \\ &= 5 - 0.7 - 0.7 \\ &= 3.6 \text{ V} \\ &= \text{logic 1} \\ V_0 &= \text{logic 1} \end{aligned}$$

Case II : $A = 0, B = 1$

Case III : $A = 1, B = 0$

Case IV : $A = 1, B = 1$

same as case (I)

For this case, transistor Q_1 works in inverse mode due to this Q_2 and Q_3 both will be ON and voltage at $V_x = V_{CE2} + V_{CE2(sat)} + V_{BE3}$

$$\begin{aligned} &= 0.2 + 0.7 \\ &= 0.9 \text{ V} \end{aligned}$$

This voltage is not sufficient to turn ON Q_4 and D_1 because it is less than 1.4 V. So Q_4 and D_1 both will be OFF and output $V_0 = V_{CE3(sat)} = 0.2$ V = logic 0.

Q.1(c) Convert JK Flip-Flop into D Flip-Flop and T Flip-Flop.


[5]

(A) Excitation table

Q_n	Q_{n+1}	J	K	D	T
0	0	0	×	0	0
0	1	1	×	1	1
1	0	×	1	0	1
1	1	×	0	1	0


1) JK to D flip-flop

$$J = D, K = \bar{D}$$

 

2) JK to T flip-flop


$$J = T, K = T$$

 

Q.1(d) Explain twisted ring counter.

[5]

(A)

 

a	b	c	d
0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1
0	0	0	0

Q.2(a) State and prove De-Morgan theorem.


[10]

(A) **Theorem :** $(A \cdot B) = \overline{\overline{A} + \overline{B}}$

Compliment of product equal to sum of their compliments.

Proof :

A	B	\overline{A}	\overline{B}	\overline{AB}	$\overline{\overline{A} + \overline{B}}$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

 


Theorem : $(\overline{A + B}) = \overline{A} \cdot \overline{B}$

Compliment of sum equal to product of their compliments.

Proof :

A	B	\overline{A}	\overline{B}	$\overline{A+B}$	$\overline{A} \cdot \overline{B}$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

 

Q.2(b) Reduce the following function using Quine Mc-Clusky method : [10]

$$f(A,B,C,D) = \sum m(2,3,5,7,10,13,15)$$

(A) Step 1 :

Decimal	A	B	C	d
2	0	0	1	0
3	0	0	1	1
5	0	1	0	1
7	0	1	1	1
10	1	0	1	0
13	1	1	0	1
15	1	1	1	1

Step 2 :

Group	Decimal	A	B	C	D
1	2	0	0	1	0
2	3	0	0	1	1
	5	0	1	0	1
	10	1	0	1	0
3	7	0	1	1	1
	13	1	1	0	1
4	15	1	1	1	1

Step 3 :

Group	Decimal	A	B	C	D
1	2,3	0	0	1	X
	2,10	X	0	1	0
2	3,7	0	X	1	1
	5,7	0	1	X	1
	5,13	X	1	0	1
3	7,15	X	1	1	1
	13,15	1	1	X	1

P_A

P_B

P_C

Group	Decimal	A	B	C	D
1	5,7,13,15	X	1	X	1
	5,13,7,15	X	1	X	1

P_D

Prime Implication Table

	m_2	m_3	m_5	m_7	m_{10}	m_{13}	m_{15}	Necessary
P_A	✓	✓						P_A
P_B	✓				✓			P_B
P_C		✓		✓				
P_D			✓	✓		✓	✓	P_D

Q.3(a) Design gray to binary code converter.



[10]

(A) Now in this case we have to do reverse i.e. convert gray codes to binary. Procedure is same as that we followed in above example.

1) Truth table :

Decimal	G ₃	G ₂	G ₁	G ₀	B ₃	B ₂	B ₁	B ₀
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
3	0	0	1	1	0	0	1	0
2	0	0	1	0	0	0	1	1
6	0	1	1	0	0	1	0	0
7	0	1	1	1	0	1	0	1
5	0	1	0	1	0	1	1	0
4	0	1	0	0	0	1	1	1
12	1	1	0	0	1	0	0	0
13	1	1	0	1	1	0	0	1
15	1	1	1	1	1	0	1	0
14	1	1	1	0	1	0	1	1
10	1	0	1	0	1	1	0	0
11	1	0	1	1	1	1	0	1
9	1	0	0	1	1	1	1	0
8	1	0	0	0	1	1	1	1

2) K-map :

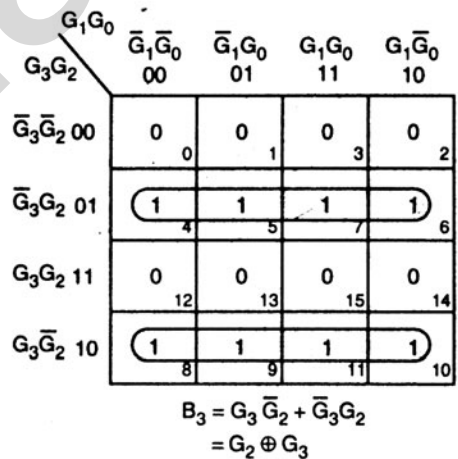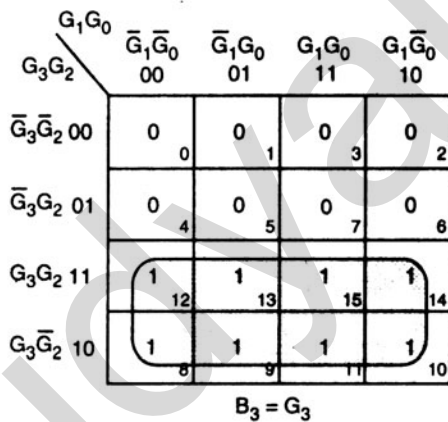


	G_1G_0	$\bar{G}_1\bar{G}_0$	\bar{G}_1G_0	G_1G_0	$G_1\bar{G}_0$
G_3G_2	00	01	11	10	
$\bar{G}_3\bar{G}_2$	00	01	11	10	
\bar{G}_3G_2	01	01	11	10	
G_3G_2	11	01	11	10	
$G_3\bar{G}_2$	10	01	11	10	

$$\begin{aligned}
 B_1 &= \bar{G}_1 (\bar{G}_3 G_2 + G_3 \bar{G}_2) \\
 &+ G_1 (\bar{G}_3 \bar{G}_2 + G_3 G_2) \\
 &= \bar{G}_1 (G_2 \oplus G_3) + G_1 (\bar{G}_2 \oplus \bar{G}_3) \\
 &= G_1 \oplus G_2 \oplus G_3
 \end{aligned}$$

	G_1G_0	$\bar{G}_1\bar{G}_0$	\bar{G}_1G_0	G_1G_0	$G_1\bar{G}_0$
G_3G_2	00	01	11	10	
$\bar{G}_3\bar{G}_2$	00	01	11	10	
\bar{G}_3G_2	01	01	11	10	
G_3G_2	11	01	11	10	
$G_3\bar{G}_2$	10	01	11	10	

$$\begin{aligned}
 B_0 &= \bar{G}_1 \bar{G}_0 (G_3 \bar{G}_2 + \bar{G}_3 G_2) + \bar{G}_1 G_0 (\bar{G}_3 \bar{G}_2 + G_3 G_2) \\
 &+ G_1 \bar{G}_0 (G_3 \bar{G}_2 + \bar{G}_3 G_2) + G_1 G_0 (\bar{G}_3 \bar{G}_2 + G_3 G_2) \\
 &= \bar{G}_1 \bar{G}_0 (G_3 \oplus \bar{G}_2) + \bar{G}_1 G_0 (\bar{G}_3 \oplus G_2) \\
 &+ G_1 \bar{G}_0 (G_3 \oplus G_2) + G_1 G_0 (\bar{G}_3 \oplus \bar{G}_2) \\
 &= (G_3 \oplus G_2) (\bar{G}_1 \bar{G}_0 + G_1 G_0) + (\bar{G}_3 \oplus G_2) (\bar{G}_1 G_0 + G_1 \bar{G}_0) \\
 &= (G_3 \oplus G_2) (\bar{G}_1 \oplus G_0) + (\bar{G}_3 \oplus G_2) (G_1 \oplus G_0) \\
 &= \bar{A} \bar{B} + \bar{A} B \\
 &= G_0 \oplus G_1 \oplus G_2 \oplus G_3
 \end{aligned}$$


3) Circuit :

 

Q.3(b) Design 4 bit synchronous converter using JK Flip-Flop.

[10]



(A)

 

Q_D	Q_C	Q_B	Q_A
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Present state Q_n	Next state Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Present state				Next state				Flip-flop input							
Q_D	Q_C	Q_B	Q_A	Q_{D+1}	Q_{C+1}	Q_{B+1}	Q_{A+1}	J_D	K_D	J_C	K_C	J_B	K_B	J_A	K_A
0	0	0	0	0	0	0	1	0	x	0	x	0	x	1	x
0	0	0	1	0	0	1	0	0	x	0	x	1	x	x	1
0	0	1	0	0	0	1	1	0	x	0	x	x	0	1	x
0	0	1	1	0	1	0	0	0	x	1	x	x	1	x	1
0	1	0	0	0	1	0	1	0	x	x	0	0	x	1	x
0	1	0	1	0	1	1	0	0	x	x	0	1	x	x	1
0	1	1	0	0	1	1	1	0	x	x	0	x	0	1	x
0	1	1	1	1	0	0	0	1	x	x	1	x	1	x	1
1	0	0	0	1	0	0	1	x	0	0	x	0	x	1	x
1	0	0	1	1	0	1	0	x	0	0	x	1	x	x	1
1	0	1	0	1	0	1	1	x	0	0	x	x	0	1	x
1	0	1	1	1	1	0	0	x	0	1	x	x	1	x	1
1	1	0	0	1	1	0	1	x	0	x	0	0	x	1	x
1	1	0	1	1	1	1	0	x	0	x	0	1	x	x	1
1	1	1	0	1	1	1	1	x	0	x	0	x	0	1	x
1	1	1	1	0	0	0	0	x	1	x	1	x	1	x	1

  

For J_C

DC \ BA	00	01	11	10
00	0	0	1	0
01	X	X	X	X
11	X	X	X	X
10	0	0	1	0

$J_C = BA$

For J_B

DC \ BA	00	01	11	10
00	0	1	X	X
01	0	1	X	X
11	0	1	X	X
10	0	1	X	X

$J_B = A$

For K_C

DC \ BA	00	01	11	10
00	X	X	X	X
01	0	0	1	0
11	0	0	1	0
10	X	X	X	X

$K_C = BA$

For K_B

DC \ BA	00	01	11	10
00	X	X	1	0
01	X	X	1	0
11	X	X	1	0
10	X	X	1	0

$K_B = A$

For J_A


DC \ BA	00	01	11	10
00	1	X	X	1
01	1	X	X	1
11	1	X	X	1
10	1	X	X	1

$J_A = 1$

For K_A

DC \ BA	00	01	11	10
00	X	1	1	X
01	X	1	1	X
11	X	1	1	X
10	X	1	1	X

$K_A = 1$

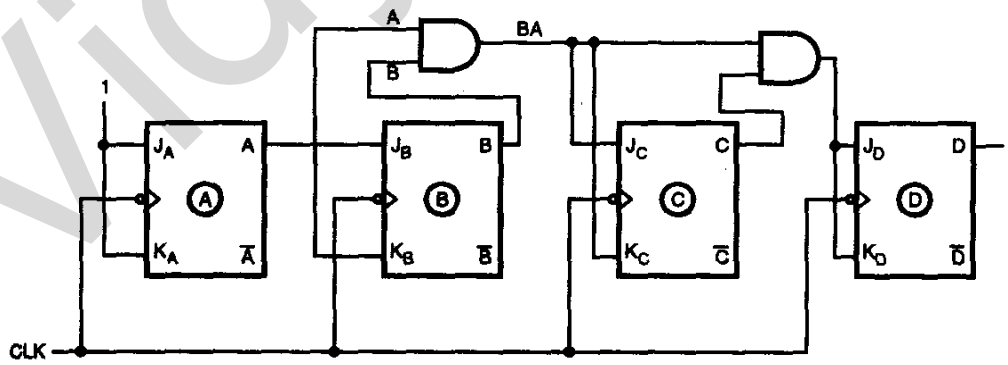


Q.4(a) Explain 4 bit bidirectional shift register.

[10]

(A) Bi-Directional Shift Register

Mode Control (M)

 

When Mode Control $M = 1$ all the 'A' AND gates are enabled and DR is shifted to lie right, when the clock pulses are applied.

When Mode Control $M = 0$ all the 'B' AND gates are enabled and DL is shifted to the left.

Q.4(b) Implement following function using :


[10]

(i) 8:1 mux, (ii) 4:1 mux, (iii) 2:1 mux


$$Y = \sum m(0, 1, 2, 3, 8, 9, 13, 14)$$

(A) (i) Using 8 : 1


Logic 0 Logic 1

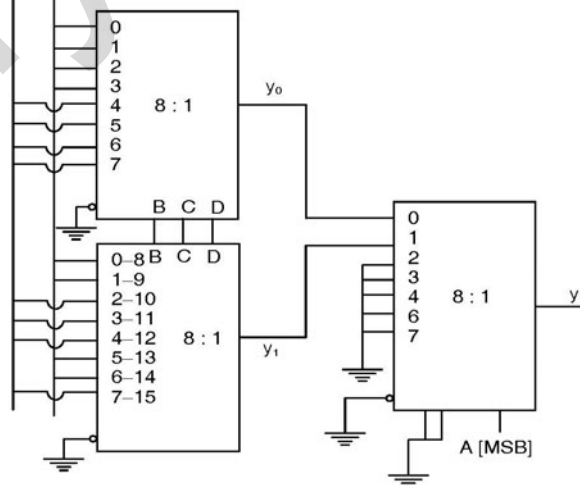

(ii) Using 4 : 1 Multiplexers :

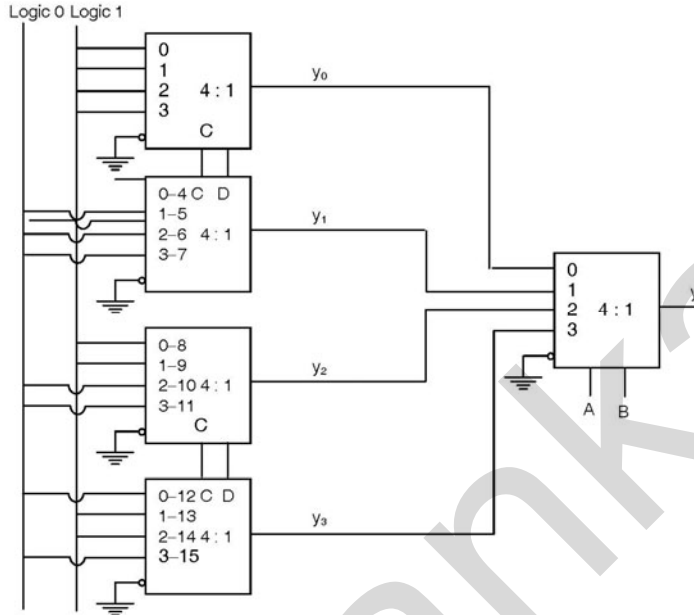


(iii) Using 2 : 1 Multiplexers :

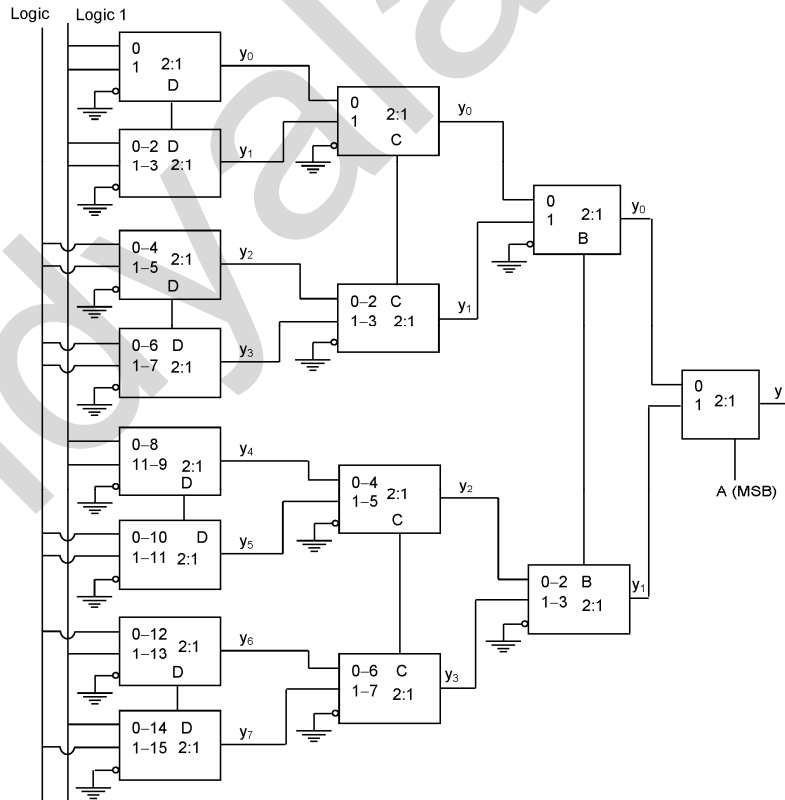

Q.5(a) Draw neat circuit diagram and explain master slave JK flip-flop [10] with NAND gates.

(A) Master Slave JK Flip Flop

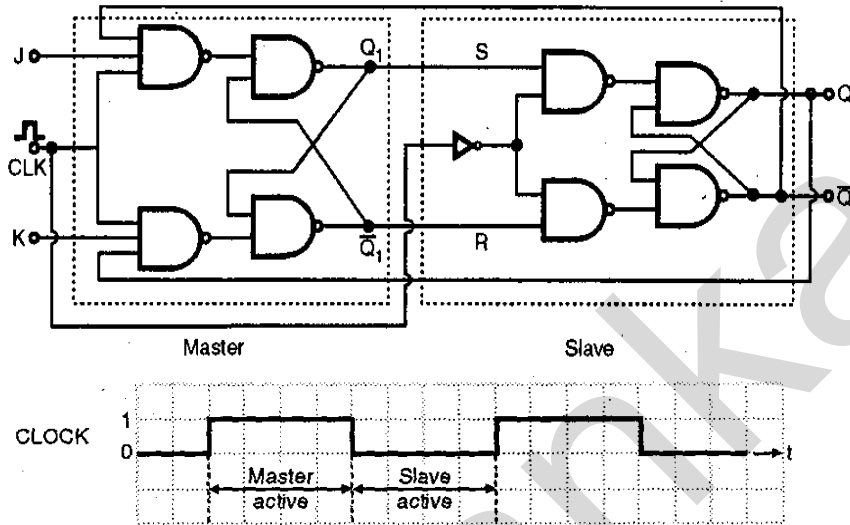

Master is positive level triggered. But due to the presence of the inverter in the clock line, the slave will respond to the negative level. Hence when the clock = 1 (positive level) the master is active and the slave is inactive, whereas when clock = 0 (low level) the slave is active and the master is inactive.

Case I : Clock = X, J = K = 0

- (i) For clock = 1, the master is active, slave inactive. As J = K = 0. Therefore, output of master, i.e., Q_1 and \bar{Q}_1 will not change. Hence the S and R inputs to the slave will remain unchanged.
- (ii) As soon as clock = 0, the slave becomes active and master is inactive. But since the S and R inputs have not changed, the slave outputs will also remain unchanged.

\therefore The outputs won't change if J = K = 0.

Case II : Clock = \square , J = K = 0

This condition has been already discussed in case f.

Case III : Clock = \square , J = 0 and K = 1.

- Clock = 1 : Master active, slave inactive.
- Therefore, outputs of the master become $Q_1 = 1$ and $\bar{Q}_1 = 0$. That means S = 0 and R = 1.
- Clock = 0 : Slave active, master inactive.

- Therefore, outputs of the slave become $Q = 0$ and $\bar{Q} = 1$.
- Again if clock = 1 : Master active, slave inactive.
Therefore, even with the changed outputs $Q = 0$ and $\bar{Q} = 1$ feedback to master, its outputs will $Q_1 = 0$ and $\bar{Q}_1 = 1$. That means $S = 0$ and $R = 1$.
- Hence with clock = 0 and slave becoming active, the outputs of slave will remain $Q = 0$ and $\bar{Q} = 1$.
- Thus we get a stable output from the Master Slave.

Case IV : Clock = \square , $J = 1, K = 0$

- Clock = 1 : Master active, slave inactive.
Therefore, outputs of master become $Q_1 = 0$ and $\bar{Q}_1 = 0$, i.e., $S = 1$, $R = 0$.
- Clock = 0 : Master inactive, slave active.
Therefore, outputs of slave become $Q = 1$ and $\bar{Q} = 0$.
- Again if clock = 1 then it can be shown that the outputs of the slave are stabilized to $Q = 1$ and $\bar{Q} = 1$.

Case V : Clock = \square , $J = 1, K = 1$.


- Clock = 1 : Master active, slave inactive.
Therefore, outputs of master will toggle. So S and R also will be inverted.
- Clock = 0 : Master inactive, slave active.
Therefore, outputs of the slave will toggle.
- These changed output are returned back to the master inputs.
- But since clock = 0, the master is still inactive. So it does not respond to these changed outputs.
- This avoids the multiple toggling which leads to the race around condition. Thus the master slave flip flop will avoid the race around condition.

Q.5(b) Design 3:8 decoder using basic logic gates.

[10]

(A) Consider B_2, B_1, B_0 are binary inputs.

$D_0 - D_7$ are Decimal outputs.

 

Functional Table :

B_2	B_1	B_0	D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Q.6(a) Explain features of VHDL.

[6]

- (A)
- VHDL has powerful constructs
 - VHDL language supports hierarchy (i.e. modelled using a set of interconnected components)
 - VHDL is not case sensitive
 - VHDL supports both synchronous and asynchronous timing models.
 - Concurrency timing and clocking can be modeled using VHDL
 - VHDL is target independent
 - VHDL supports design library
 - VHDL has flexible design methodologies i.e. TOP DOWN, BOTTOM UP, MIXED
 - The logical behavior and timing behavior of the design can be modeled using VHDL.
 - VHDL is not technology specific i.e. VHDL is not dependent on the specific manufacturer i.e. XILINX or LATTICE.
 - VHDL's technology specific feature allows to specify components from various vendors
 - VHDL also allows the user to specify his own data type and component
 - VHDL is publicly available and has no proprietary.

Q.6(b) Explain BCD adder with suitable example.

[7]


(A) 1. $6 \rightarrow 0110$
 $+ 5 \rightarrow 0101$
 $===$
 $11 \quad 1011$
 $0110 \rightarrow$ add 6 if result is invalid.

$1 \quad 0001$

2. $8 \rightarrow 1000$
 $+9 \rightarrow +1001$
 $===$
 $17 \quad 1 \quad 0001$
 $+ 0110 \rightarrow$ add 6

$1 \quad 0111$

$1 \quad 7$

 

Q.6(c) Compare FPGA and CPLD.

[7]

(A)

	CPLDs	FPGAs
Architecture	Large, wide fan-in blocks of AND-OR logic	Array of small logic blocks surrounded by I/O
Applications	Bus interfaces Complex state machines Fast memory interfaces Wide decoders PAL-device integration	Logic consolidation Board integration Replace obsolete devices Simple state machines Complex controllers/interfaces
Key Attributes	Fast pin-to-pin performance Predictable timing Easy to use	Very high density Lots of I/Os and flip-flops Generally lower power SRAM devices are reprogrammable
Gate Capacity	300-6,000 gates	800-100,000 gates
Design Timing	Fixed, PAL-like Very fast pin-to-pin performance	Application dependent Very high shift frequencies
Number of I/Os	30-200	50-400
Number of Flip-flops	30-200	100-5,500
Process Technology	EPROM EEPROM FLASH	SRAM Anti-fuse EEPROM
In-System Programmable	Some EEPROM- and FLASH-based devices	SRAM-based devices and some EEPROM-based devices
One-Time Programmable (OTP)	EPROM devices in plastic packages. Some EEPROM- and FLASH-based devices	All anti-fuse-based devices
Power Consumption	0.5-2.0W static 0.5-4.0W dynamic	Very low static Dynamic consumption is application dependent, 0.1-2W typical

