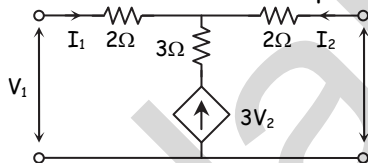


- N.B.:** (1) Question No. 1 is **compulsory**.
 (2) Attempt any **three** questions out of remaining questions.
 (3) Use Smith Chart wherever required.
 (4) Assume suitable **data** if required.

1. (a) Test whether $P(s) = s^5 + 12s^4 + 45s^3 + 60s^2 + 44s + 48$ is Hurwitz polynomial. **[5]**


(b) The constants of a transmission line are $R = 6 \Omega/\text{km}$, $L = 2.2 \text{ mH}/\text{km}$, $G = 0.25 \times 10^{-6} \text{ S}/\text{km}$, $C = 0.005 \times 10^{-5} \text{ F}/\text{km}$. Determine the characteristic impedance, propagation constant and attenuation constant at 1 KHz. **[5]**

(c) Determine the short circuit admittance parameters of the network shown : **[5]**




(d) State and prove final value theorem of Laplace transform. **[5]**

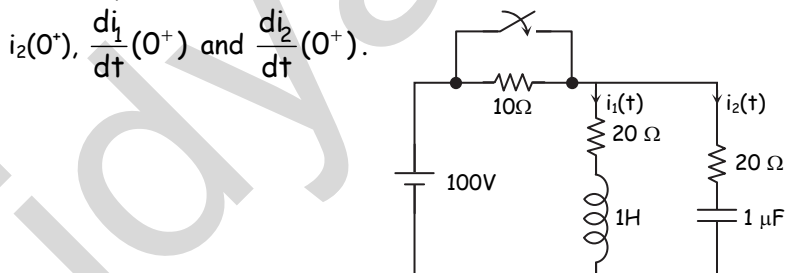2. (a) The network shown in figure, a steady state is reached with the switch open. At $t = 0$, the switch is closed. Determine $V_c(0^-)$, $i_1(0^-)$, $i_2(0^-)$, $\frac{di_1}{dt}(0^+)$ and $\frac{di_2}{dt}(0^+)$. **[10]**




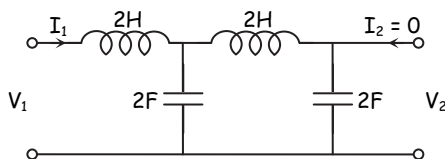(b) Find the network functions $\frac{V_1}{I_1}$, $\frac{V_2}{I_1}$, $\frac{V_2}{V_1}$ for the network shown : **[5]**




(c) In the circuit shown in figure, find V_x .

[5]

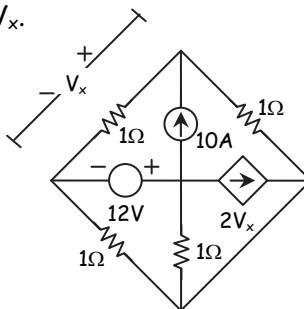

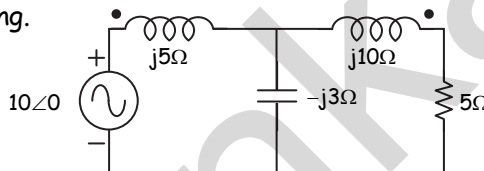3. (a) Find the voltage across $5\ \Omega$ resistor in the network shown below. If $K = 0.8$ is coefficient of coupling. [8]




(b) Check the positive real function : [8]


(i) $F(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}$ (ii) $F(s) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$

(c) List the types of damping in series R-L-C circuit and mention the condition for each damping. [4]

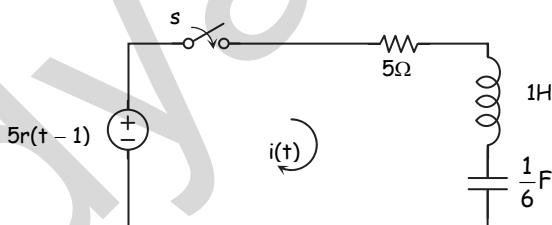
4. (a) For the network shown, determine the current $i(t)$ when the switch is closed at $t = 0$ with zero initial conditions. [8]



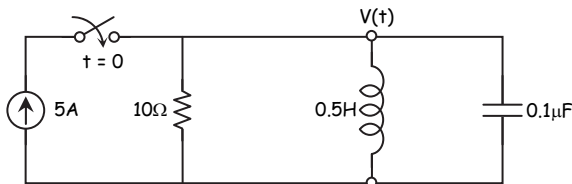(b) In the given network switch is closed at $t = 0$. Solve for V , $\frac{dV}{dt}$, $\frac{d^2V}{dt^2}$ at $t = 0^+$. [8]



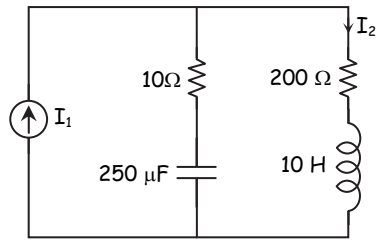(c) Obtain pole-zero plot for $\frac{I_2}{I_1}$.




[4]

5. (a) Synthesize the driving point function using Foster - I and Foster - II form :

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

(b) Obtain hybrid parameter of the inter-connected network.


[10]

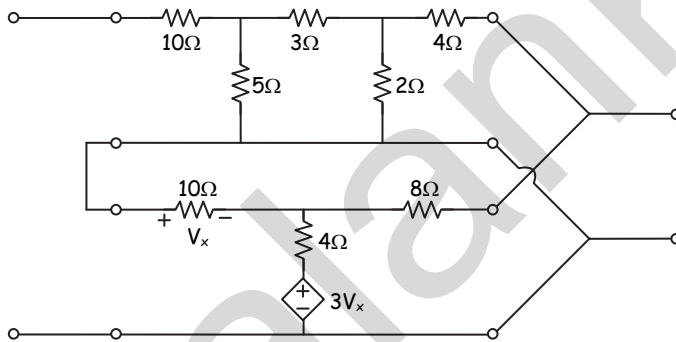

6. (a) The characteristic impedance of a high frequency line is 100Ω . If its terminated by a load impedance of $100 + j100 \Omega$. Using smith chart, find out : (i) VSWR, (ii) Reflection coefficient, (iii) Impedance at $(1/10)^{th}$ of wave length away from load, (iv) VSWR minimum and VSWR maximum away from the load.

(b) Find the characteristic impedances, cut-off frequency and passband frequency for given network.

[5]

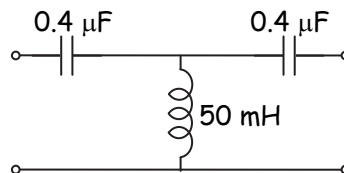

(c) Explain various types of filters.

[5]

