

Q.1(a) Test whether $P(s) = s^5 + 12s^4 + 45s^3 + 60s^2 + 44s + 48$ is Hurwitz [5] polynomial.

(A) $P(s) = s^5 + 12s^4 + 45s^3 + 60s^2 + 44s + 48$

s^5	1	45	44
s^4	12	60	48
s^3	40	40	0
s^2	48	48	
s^1	0	0	

As complete row becomes zero we will form an auxiliary equation.

$$A(s) = 48s^2 + 48$$

$$A'(s) = 96s + 0$$

Replacing zeroth row with $A'(s)$

s^5	1	45	44
s^4	12	60	48
s^3	40	40	0
s^2	48	48	
s^1	96	0	
s^0	48		

As all the elements in the 1st columns are positive given f^n is a Hurwitz polynomial.

Q.1(b) The constants of a transmission line are $R = 6 \Omega/\text{km}$, [5]

$L = 2.2 \text{ mH}/\text{km}$, $G = 0.25 \times 10^{-6} \text{ S}/\text{km}$, $C = 0.005 \times 10^{-5} \text{ F}/\text{km}$.

Determine the characteristic impedance, propagation constant and attenuation constant at 1 KHz.

(A) Given : $R = 6 \Omega / \text{km}$, $L = 2.2 \text{ mH}/\text{km}$, $G = 0.25 \times 10^{-6} \text{ S} / \text{km}$

$C = 0.005 \times 10^{-5} \text{ F}/\text{km}$, $F = 1\text{KHz}$

To find : Z_0, γ, α

$$\begin{aligned} z &= R + j\omega L \\ &= 6 + j2\pi \times 10^3 \times 2.2 \times 10^{-3} \\ &= 6 + j13.82 \\ z &= 15.06 \angle 66.53^\circ \end{aligned}$$


$$\begin{aligned}
 y &= G + j\omega C \\
 &= 0.25 \times 10^{-6} + j2\pi 10^3 \times 0.005 \times 10^{-5} \\
 &= 0.25 \times 10^{-6} + j 3.14 \times 10^{-4} \\
 &= 3.14 \times 10^{-4} \angle 89.95^\circ
 \end{aligned}$$

$$\begin{aligned}
 \text{Characteristic impedance} = z_0 &= \sqrt{\frac{z}{y}} = \sqrt{\frac{15.06 \angle 66.53^\circ}{3.14 \times 10^{-4} \angle 89.95^\circ}} \\
 &= 219.00 \angle 11.71^\circ \Omega
 \end{aligned}$$


Propagation constant

$$\begin{aligned}
 \gamma &= \sqrt{z \cdot y} = \sqrt{(15.06 \angle 66.53)(3.14 \times 10^{-4} \angle 89.95)} \\
 \gamma &= 0.014 + j 0.067 / \text{km} \\
 \gamma &= \alpha + j\beta \\
 \alpha &= 0.014 \text{ Np/km,} \\
 \beta &= 0.067 \text{ rad/km}
 \end{aligned}$$

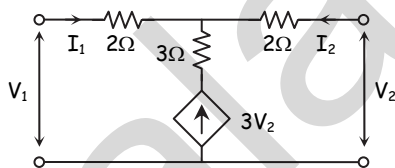Q.1(c) Determine the short circuit admittance parameters of the network [5]
shown :



(A)

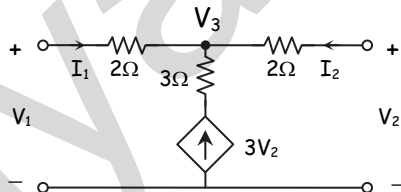

Apply RCL at V_3

$$\frac{V_3 - V_1}{2} + \frac{V_3 - V_2}{2} = 3V_2$$

$$V_3 \left(\frac{1}{2} + \frac{1}{2} \right) = 3V_2 + \frac{V_2}{2} + \frac{V_1}{2}$$

$$V_3 = 0.5 V_1 + 3.5 V_2 \quad \dots(1)$$

Apply KCL at V_1

$$I_1 = \frac{V_1 - V_3}{2}$$

$$I_1 = \frac{V_1}{2} = \frac{1}{2} (0.5V_1 + 3.5V_2)$$

$$I_1 = V_1(0.25) - V_2(1.75)$$

Comparing with $I_1 = y_{11}V_1 + y_{12}V_2$

$$y_{11} = 0.25 \text{ } \Omega^{-1} \quad y_{12} = -1.75 \text{ } \Omega^{-1}$$

Apply KCL at V_2

$$I_2 = \frac{V_2 - V_3}{2}$$

$$I_2 = \frac{V_2}{2} - \frac{1}{2}(0.5V_1 + 3.5V_2)$$

$$I_2 = -0.25V_1 - 1.25V_2$$

$$y_{21} = -0.25 \text{ } \Omega^{-1}, \quad y_{22} = -1.25 \text{ } \Omega^{-1}$$

Q.1(d) State and prove final value theorem of Laplace transform. [5]

(A) If $L\{f(t)\} = F(s)$ then $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$

Proof : We know that

$$L\{f'(t)\} = sF(s) - f(0)$$

$$sF(s) = L\{f'(t)\} + f(0)$$

$$sF(s) = \lim_{s \rightarrow 0} \int_0^{\infty} f'(t)e^{-st} dt + f(0)$$

$$= \int_0^{\infty} \lim_{s \rightarrow 0} [f'(t)e^{-st}] dt + f(0)$$

$$= \int_0^{\infty} f'(t) dt + f(0)$$


$$= [f(t)]_0^{\infty} + f(0)$$

$$= \lim_{t \rightarrow \infty} f(t) - f(0) + f(0)$$

$$= \lim_{t \rightarrow \infty} f(t)$$

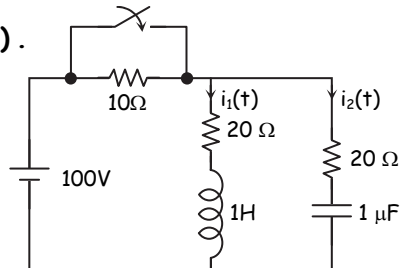**Q.2(a) The network shown in figure, a steady state is reached with the [10]
switch open. At $t = 0$, the switch is closed. Determine $V_c(0^-)$,**

$i_1(0^+)$, $i_2(0^+)$, $\frac{di_1}{dt}(0^+)$ and $\frac{di_2}{dt}(0^+)$.



(A) Step 1: At $t = 0^-$, switch is open
 $i_2(0^-) = 0$

finding $i_1(0^-)$

$$100 - 10 i_1 - 20 i_1 = 0$$


$$100 = 30 i_1$$

$$\therefore i_1 = \frac{100}{30} = \frac{10}{3} \text{ A}$$

$$\therefore i_1(0^-) = \frac{10}{3} \text{ A}$$

$$V_C(0^-) = 20 \times i_1(0^-) = 20 \times \frac{10}{3}$$

$$V_C(0^-) = \frac{200}{3} \text{ V}$$

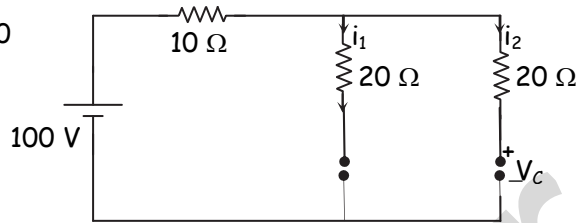

Step 2: At $t = 0^+$


$$i_1(0^+) = \frac{10}{3} \text{ A}$$

Apply KVL to the outer loop

$$100 - 20i_2 - \frac{200}{3} = 0$$

$$20 i_2 = 100 - \frac{200}{3}$$

$$i_2(0^+) = 1.67 \text{ A}$$

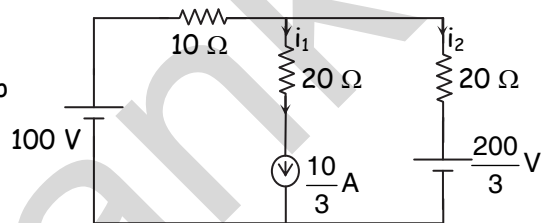

Step 3: At $t > 0$

Apply KVL to loop (1)

$$100 - 20 i_1 - \frac{di_1}{dt} = 0$$

$$\frac{di_1}{dt} = 100 - 20 i_1(0^+)$$

$$= 100 - \frac{20 \times 10}{3}$$

$$\frac{di_1}{dt} = 33.33 \text{ A/s}$$


Apply KVL to outer loop

$$100 - 20 i_2 - \frac{1}{10^{-6}} \int i_2 dt = 0$$

Differentiate w.r.t. t

$$0 - 20 \frac{di_2}{dt} - 10^6 i_2 = 0$$

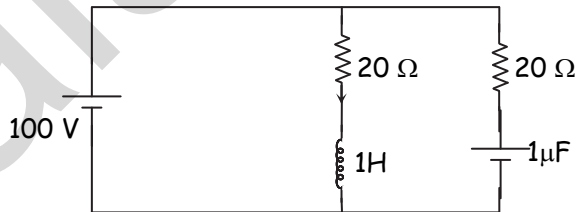
$$-20 \frac{di_2(0^+)}{dt} = 10^6 i_2(0^+)$$




$$\frac{di_2}{dt} = \frac{-10^6(1.67)}{20}$$

$$\frac{di_2}{dt} = -83500 \text{ A/s}$$

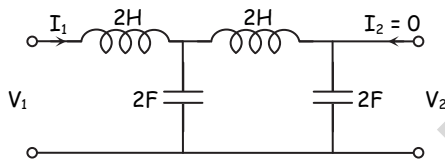Q.2(b) Find the network functions $\frac{V_1}{I_1}$, $\frac{V_2}{I_1}$, $\frac{V_2}{V_1}$ for the network shown : [5]



(A)

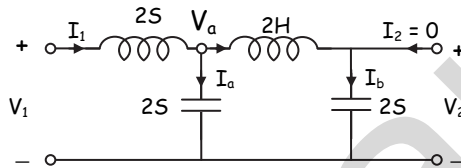

Let $V_2 = 1$

$$I_b = V_2 \times 2S$$

$$V_a = V_2 + I_b \cdot 2S$$

$$= 1 + 2S \cdot 2S$$

$$V_a = 1 + 4S^2$$

$$I_a = V_a \cdot 2S$$

$$= (1 + 4S^2)2S$$

$$I_a = 2S + 8S^3$$

$$I_1 = I_a + I_b$$

$$= 2S + 8S^3 + 2S$$

$$I_1 = 8S^3 + 4S$$

$$V_1 = V_a + I_1 \cdot 2S$$

$$= 1 + 4S^2 + (8S^3 + 4S)2S$$

$$= 1 + 4S^2 + 16S^4 + 8S^2$$


$$V_1 = 16S^4 + 12S^2 + 1$$

$$\frac{V_1}{I_1} = \frac{16S^4 + 12S^2 + 1}{8S^3 + 4S}$$


$$\frac{V_2}{I_1} = \frac{1}{8S^3 + 4S} \quad \& \quad \frac{V_2}{V_1} = \frac{1}{16S^4 + 12S^2 + 1}$$

Q.2(c) In the circuit shown in figure, find V_x .

[5]

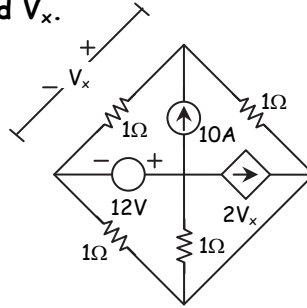

(A)

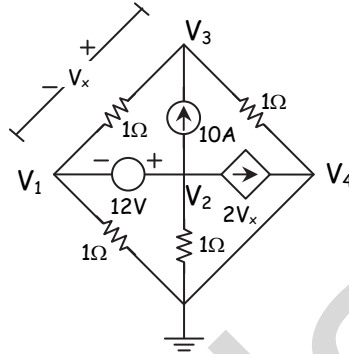

$$V_4 = 0 \text{ V}$$

$$V_x = V_1 - V_3 \quad \dots(1)$$

Relation between V_1 & V_2

$$V_2 - V_1 = 12$$

$$-V_1 + V_2 + 0V_3 = 12 \quad \dots(2)$$

Supernode equation

$$\frac{V_1 - V_3}{1} + \frac{V_1}{1} + \frac{V_2}{1} + 10 + 2V_x = 0$$

$$V_1 - V_3 + V_1 + V_2 + 10 + 2(V_1 - V_3) = 0 \quad \dots(\text{from 1})$$

$$4V_1 + V_2 - 3V_3 = -10 \quad \dots(3)$$

KCL to V_3

$$\frac{V_3 - V_1}{1} + \frac{V_3}{1} = 10$$

$$-V_1 + 0V_2 + 2V_3 = 10 \quad \dots(4)$$

Solving (2), (3) & (4)

$$V_1 = -2 \text{ V}$$

$$V_2 = 10 \text{ V}$$

$$V_3 = 4 \text{ V}$$


$$V_x = V_1 - V_3$$

$$V_x = -2 - 4$$

$$V_x = -6 \text{ V}$$

Q.3(a) Find the voltage across $5\ \Omega$ resistor in the network shown below. [8]

If $K = 0.8$ is coefficient of coupling.

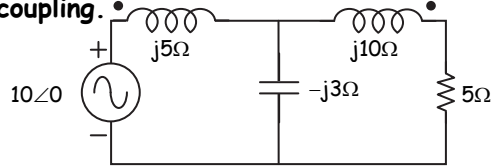


(A) For a magnetically coupled circuit,

$$M = K\sqrt{5(10)}$$

$$X_m = K\sqrt{X_{L_1} X_{L_2}} = 0.8\sqrt{5(10)} = 5.66\ \Omega$$

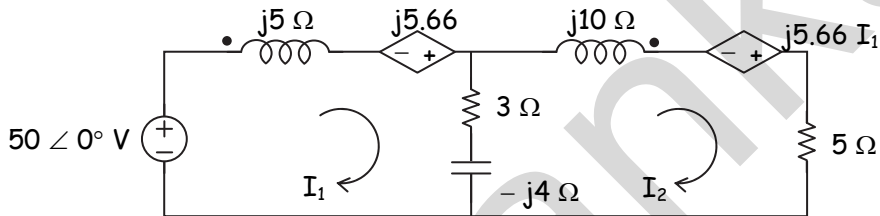The equivalent circuit in terms of dependent sources can be drawn as



Applying KVL to Mesh 1,

$$50\ \angle\ 0^\circ - j5I_1 - 3(I_1 - I_2) + j4(I_1 - I_2) + j5.66I_2 = 0$$

$$50\ \angle\ 0^\circ = (3 + j1)I_1 - (3 + j1.66)I_2 \quad \dots (1)$$

$$(3 + j1)I_2 + (-3 - j1.66)I_2 = 50\ \angle\ 0^\circ$$

Applying KVL to Mesh 2,

$$j4(I_2 - I_1) - 3(I_2 - I_1) - j10I_2 + j5.66I_1 - 5I_2 = 0$$

$$j4I_2 - j4I_1 - 3I_2 + 3I_1 - j10I_2 + j5.66I_1 - 5I_2 = 0$$

$$-j4I_2 + j4I_1 + 3I_2 - 3I_1 + j10I_2 - j5.66I_1 + 5I_2 = 0$$

$$(-3 - j1.66)I_1 + (8 + j6)I_2 = 0 \quad \dots (2)$$

By Cramer's rule,

$$I_2 = \frac{\begin{vmatrix} 3 + j1 & 50\ \angle\ 0^\circ \\ -3 - j1.66 & 0 \end{vmatrix}}{\begin{vmatrix} 3 + j1 & -3 - j1.66 \\ -3 - j1.66 & 8 + j6 \end{vmatrix}} = 8.62\ \angle\ -24.79^\circ\ \text{A}$$

$$V = 5I_2 = 5(8.62\ \angle\ -24.79^\circ) = 43.1\ \angle\ -24.79^\circ\ \text{V}$$

Q.3(b) Check the positive real function :

[8]

$$(i) F(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14} \quad (ii) F(s) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$$

$$(A) (i) F(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}$$

$$\text{Step 1 : Let } F(s) = \frac{N(s)}{D(s)} = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}$$

$$F(s) = \frac{(s+5)(s+1)}{(s+7)(s+2)}$$

The function $f(s)$ has poles at $s = -7$ & $s = -2$ & zeros at $s = -5$ and $s = -1$
 \therefore All the poles & zeros are in the left half of s -plane.

Step 2 : As there is no pole on jw axis, the residue test is not carried out.

Step 3 : Even part of $N(s) = m_1 = s^2 + 5$

Odd part of $N(s) = n_1 = 6s$

Even part of $D(s) = m_2 = s^2 + 14$

Odd part of $D(s) = n_2 = 9s$

$$A(w^2) = m_1 m_2 - n_1 n_2 = (s^2 + 5)(s^2 + 14) - (6s)(9s) \Big|_{s=jw}$$

$$= s^4 - 35s^2 + 70 \Big|_{s=jw}$$

$$\therefore A(w^2) = w^4 + 35w^2 + 70$$

$A(w^2)$ is positive for all $w \geq 0$

As all the three conditions are satisfied, the function is a positive real function.

$$(ii) F(s) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$$

$$\text{Step 1 : Let } F(s) = \frac{N(s)}{D(s)} = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$$

$$F(s) = \frac{s^3 + 6s^2 + 7s + 3}{(s+1)^2}$$

From above both the poles are lying at $s = -1$

Now we will check for $N(s)$

$$N(s) = s^3 + 6s^2 + 7s + 3$$

The Routh array of $N(s)$ is given by

s^3	1	7
s^2	6	3
s^1	$\frac{39}{6}$	0
s^0	3	

As all elements in 1st column are +ve, $N(s)$ is Hurwitz polynomial.

\therefore 1st condition is satisfied.

Step 2 : As there is no pole on jw axis, residue test need not to be carried out.

Step 3 : Even part of $N(s) = m_1 = 6s^2 + 3$

Odd part of $N(s) = n_1 = s^3 + 7s$

Even part of $D(s) = m_2 = s^2 + 1$

Odd part of $D(s) = n_2 = 2s$

$$\begin{aligned} A(w^2) &= m_1 m_2 - n_1 n_2 \\ &= (6s^2 + 3)(s^2 + 1) - (s^3 + 7s)(2s) \Big|_{s=jw} \\ &= 4s^4 - 5s^2 + 3 \Big|_{s=jw} \end{aligned}$$





$$A(w^2) = 4w^4 + 5w^2 + 3$$

\therefore We can say that $A(w^2)$ is positive for all $w \geq 0$

As all three conditions are satisfied, function $f(s)$ is a positive real function.


Q.3(c) List the types of damping in series R-L-C circuit and mention the condition for each damping. [4]

(A)

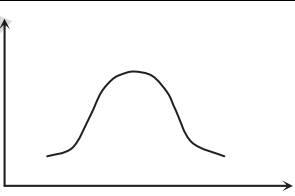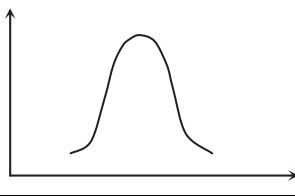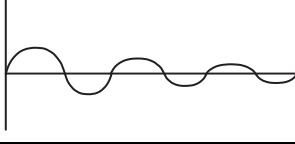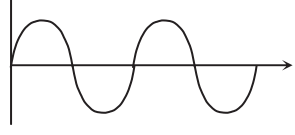	Nature of Roots	System	Response
1.	Negative Real unequal	Over damped $k_1 e^{p_1 t} + k_2 e^{p_2 t}$	
2.	Negative Real equal	Critically damped $k_1 e^{p t} + k_2 t e^{p t}$	
3.	Complex conjugate	Underdamped $e^{-\alpha t} [k_1 \cos \omega t + k_2 \sin \omega t]$	
4.	Conjugate imaginary	Oscillatory $k_1 \cos \omega t + k_2 \sin \omega t$	

where $\alpha = \frac{R}{2L}$ and $\omega_0 = \frac{1}{\sqrt{LC}}$

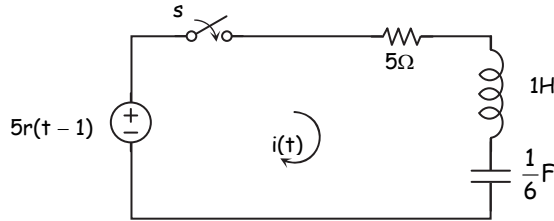Q.4(a) For the network shown, determine the current $i(t)$ when the switch is closed at $t = 0$ with zero initial conditions. [8]




(A) Step 1 At $t = 0^-$, switch is open

$$i(0^-) = 0 \text{ A}$$

$$V_c(0^-) = 0 \text{ V}$$

Step 2 At $t > 0$, switch is closed.

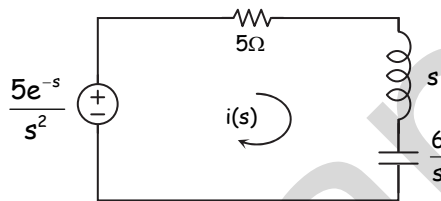

Applying KVL

$$5 \frac{e^{-s}}{s^2} - 5i(s) - s i(s) - \frac{6}{s} i(s) = 0$$

$$\frac{5e^{-s}}{s^2} = i(s) \left(5 + s + \frac{6}{s} \right)$$

$$\frac{5e^{-s}}{s^2} = \frac{5s + s^2 + 6}{s} i(s)$$

$$(s^2 + 5s + 6) i(s) = \frac{5e^{-s}}{s}$$

$$i(s) = \frac{5e^{-s}}{s(s^2 + 5s + 6)}$$

$$i(s) = \frac{5e^{-s}}{s(s+3)(s+2)}$$

Let $i_1(s) = \frac{1}{s(s+3)(s+2)} = \frac{A}{s} + \frac{B}{s+3} + \frac{C}{s+2}$

$$1 = A(s+3)(s+2) + B s(s+2) + C s(s+3)$$

$$A = \frac{1}{6}, \quad B = \frac{1}{3}, \quad C = -\frac{1}{2}$$

$$i(C) = 5e^{-s} \times i_1(s)$$

$$= 5e^{-s} \left[\frac{1}{6s} + \frac{1}{3(s+3)} - \frac{1}{2(s+2)} \right]$$


$$i(s) = \frac{5e^{-s}}{6s} + \frac{5e^{-s}}{3(s+3)} - \frac{5e^{-s}}{2(s+2)}$$

Taking inverse laplace transform

$$i(t) = \frac{5}{6}u(t-1) + \frac{5}{3}e^{-3(t-1)}u(t-1) - \frac{5}{2}e^{-2(t-1)}u(t-1)$$

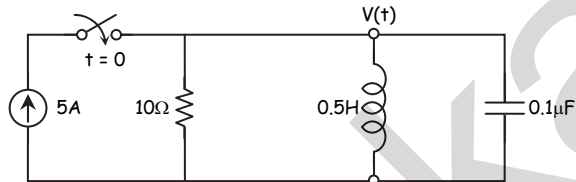Q.4(b) In the given network switch is closed at $t = 0$. Solve for V , $\frac{dV}{dt}$, [8]

$$\frac{d^2V}{dt^2} \text{ at } t = 0^+$$




(A) Step 1: At $t = 0^-$, switch is open.

$$i_L(0^-) = 0 \text{ A}$$

$$V_C(0^-) = 0 \text{ V} \text{ \& } V(0^-) = 0 \text{ V}$$


Step 2: At $t = 0^+$, switch is closed.

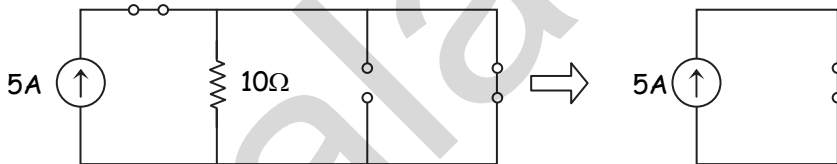

$$i_L(0^+) = 0 \text{ A}$$

$$V_1(0^+) = 0 \text{ V}, \quad V(0^+) = 0 \text{ V}$$

Step 3: At $t > 0$

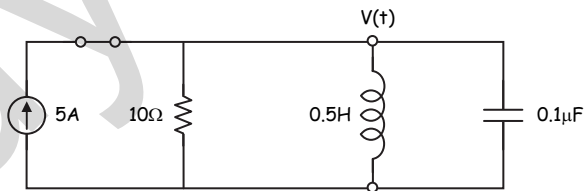

Applying KCL to V

$$\frac{V}{10} + \frac{1}{0.5} \int V dt + 0.1 \times 10^{-6} \frac{dV}{dt} = 5 \quad \dots(1)$$

At $t = 0^+$

$$\frac{V(0^+)}{10} + 0 + 0.1 \times 10^{-6} \frac{dV}{dt}(0^+) = 5$$

$$0.1 \times 10^{-6} \frac{dV}{dt}(0^+) = 5 - 0$$

$$\frac{dV}{dt}(0^+) = \frac{5}{0.1 \times 10^{-6}}$$

$$\frac{dV}{dt}(0^+) = 50 \times 10^{+6} \text{ v/s}$$

Diff. equation (1) w.r.t. t


$$\frac{dV}{10 dt} + \frac{1}{0.5} V(0^+) + 0.1 \times 10^{-6} \frac{d^2V}{dt^2} = 0$$

$$0.1 \times 10^{-6} \frac{d^2V}{dt^2} = \frac{-dV}{10 dt}$$

$$\frac{d^2V}{dt^2} = -\frac{50 \times 10^6}{10 \times 0.1 \times 10^{-6}}$$

$$\frac{d^2V}{dt^2} = -50 \times 10^{12} \text{ V/s}^2$$

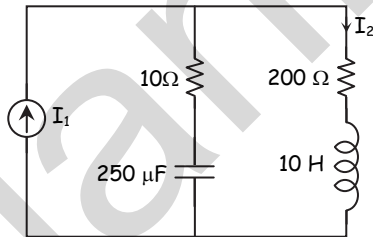Q.4(c) Obtain pole-zero plot for $\frac{I_2}{I_1}$.



[4]

(A) By C.D.R.

$$I_2 = \frac{\frac{4000}{S} + 10}{\frac{4000}{S} + 10 + 200 + 10S} \times I_1$$

$$\frac{I_2}{I_1} = \frac{\frac{4000 + 10S}{S}}{\frac{4000 + 10S + 200S + 10S^2}{S}}$$

$$\frac{I_2}{I_1} = \frac{4000 + 10S}{10S^2 + 210S + 4000}$$


$$\frac{I_2}{I_1} = \frac{10(S + 400)}{10(S^2 + 21S + 400)}$$


$$\frac{I_2}{I_1} = \frac{S + 400}{S^2 + 21S + 400}$$

$$Z_1 = -400$$

$$P_1 = -10.5 + 17.02j$$

$$P_2 = -10.5 - 17.02j$$

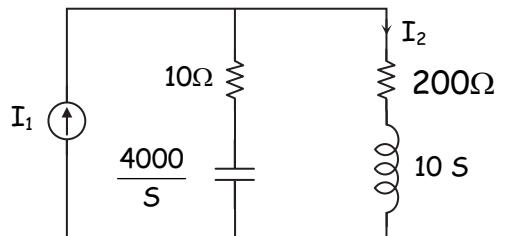

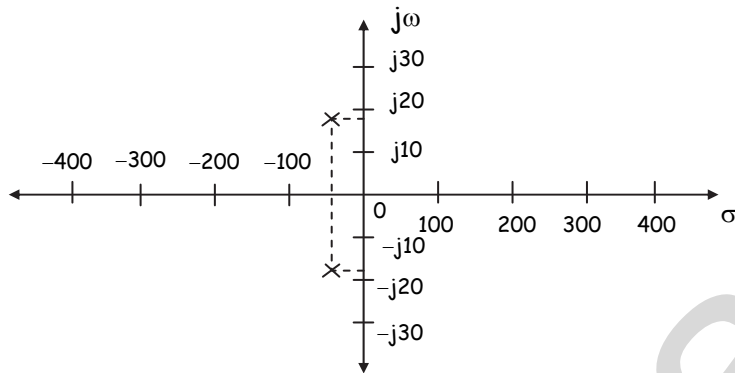

Q.5(a) Synthesize the driving point function using Foster-I and Foster-II [10]

form : $Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$

(A) Foster – I form :

A degree of numerator is greater than degree of denominator, division is first carried out.

$$Z(s) = \frac{4(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)} = \frac{4s^4 + 40s^2 + 36}{s^3 + 4s}$$

$$s^3 + 4s \overline{) 4s^4 + 40s^2 + 36}$$

$$\underline{4s^4 + 16s^2}$$

$$24s^2 + 36$$

$$\therefore Z(s) = \text{Quotient} + \frac{\text{Remainder}}{\text{Diviser}} = 4s + \frac{24s^2 + 36}{s^3 + 4s} = 4s + \frac{24s^2 + 36}{s(s^2 + 4)}$$

By partial fraction expansion

$$Z(s) = 4s + \frac{k_0}{s} + \frac{2k_1 s}{s^2 + 4}$$

$$k_0 = sz(s) \Big|_{s=0} = \frac{4(1)(9)}{4} = 9$$

$$k_1 = \frac{(s^2 + 4)z(s)}{2s} \Big|_{s^2=-4} = \frac{4(-4 + 1)(-4 + 9)}{2(-4)} = \frac{15}{2}$$

$$Z(s) = 4s + \frac{9}{s} + \frac{15s}{s^2 + 4}$$

1st term $\Rightarrow 4s \Rightarrow$ inductor of 4H

2nd term $\Rightarrow \frac{9}{s} \Rightarrow$ capacitor of $\frac{1}{9}$ F

3rd term \Rightarrow parallel LC network


For parallel LC network

$$Z_{LC}(s) = \frac{\left(\frac{1}{C}\right)_s}{s^2 + \frac{1}{LC}}$$

Comparing the terms

$$\therefore C = \frac{1}{15} \text{ F and } L = \frac{15}{4} \text{ H}$$

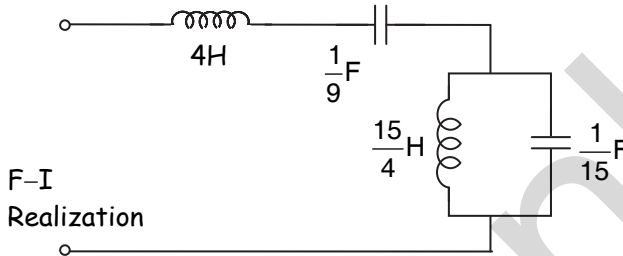\therefore Corresponding network is as follows.



Foster II form :

It is obtain by partial fraction expansion of admittance function

$$Y(s) = \frac{s(s^2 + 4)}{4(s^2 + 1)(s^2 + 9)}$$

By partial fraction expansion

$$Y(s) = \frac{2k_1 s}{s^2 + 1} + \frac{2k_2 s}{s^2 + 9}$$

$$k_1 = \frac{(s^2 + 1)}{2s} Y(s) \Big|_{s^2 = -1} = \frac{(-1 + 4)}{8(-1 + 9)} = \frac{3}{64}$$

$$k_2 = \frac{s^2 + 9}{2s} Y(s) \Big|_{s^2 = -9} = \frac{(-9 + 4)}{8(-9 + 1)} = \frac{5}{64}$$


$$Y(s) = \frac{\left(\frac{3}{32}\right)s}{s^2 + 1} + \frac{\left(\frac{5}{32}\right)s}{s^2 + 9}$$

Above two terms presents admittance of series LC network for series LC

$$\text{network} \Rightarrow Y_{LC}(s) = \frac{\left(\frac{1}{L}\right)_s}{s^2 + \frac{1}{LC}}$$

\therefore By comparison
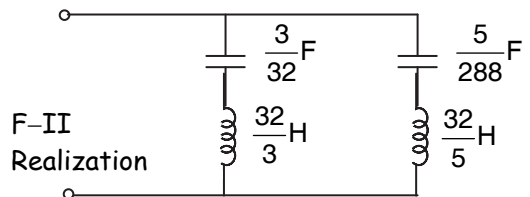
$$L_1 = \frac{3L}{3} \text{ H} \quad C_1 = \frac{3}{32} \text{ F}$$




$$L_2 = \frac{32}{5} \text{H} \quad C_2 = \frac{5}{288} \text{F}$$

Corresponding network is as shown.

Q.5(b) Obtain hybrid parameter of the inter-connected network.

[10]

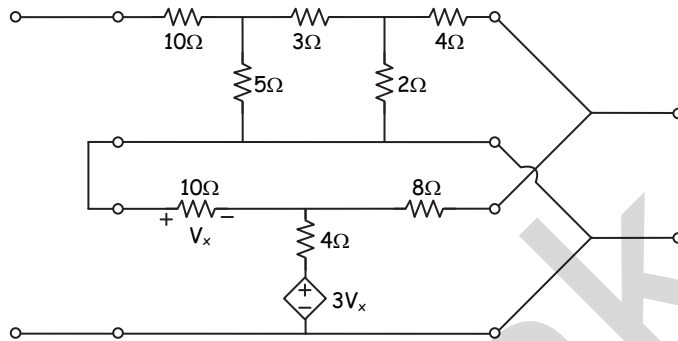

(A) Separate the two networks

1st network

$$V_x = 10 I_1$$

Apply KVL to loop of I_1

$$V_1 - 10I_1 - 4(I_1 + I_2) - 3V_x = 0$$

$$V_1 = 10 I_1 + 4(I_1 + I_2) + 3(10I_1)$$

$$V_1 = 10I_1 + 4I_1 + 4I_2 + 30I_1$$

$$V_1 = 44I_1 + 4I_2$$

Comparing with $V_1 = z_{11} I_1 + z_{12}I_2$

$$\therefore z_{11} = 44\Omega \quad z_{12} = 4\Omega$$

Apply KVL to loop of I_2

$$V_2 - 8I_2 - 4(I_2 + I_1) - 3V_x = 0$$

$$V_2 = 8I_2 + 4(I_2 + I_1) + 3(10I_1)$$

$$V_2 = 34I_1 + 12I_2$$

Comparing with

$$V_2 = z_{21}I_1 + z_{22} I_2$$

$$\therefore z_{21} = 34 \Omega \quad z_{22} = 12\Omega$$

$$\Delta Z = z_{11} z_{22} - z_{21} z_{12} = 44 \times 12 - 34 \times 4$$


$$\Delta Z = 392$$

Now finding h-parameters from Z-parameter

$$h'_{11} = \frac{\Delta Z}{z_{22}} = \frac{392}{12} = 32.66$$


$$h''_{12} = \frac{z_{12}}{z_{22}} = \frac{4}{12} = 0.333$$
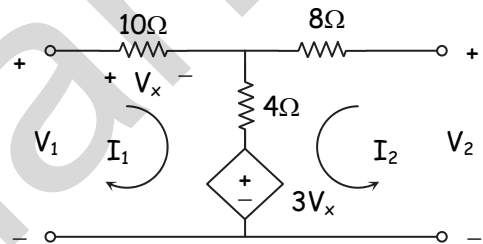
$$h'_{21} = \frac{-z_{21}}{z_{22}} = \frac{-34}{12} = -2.833$$



$$h'_{22} = \frac{1}{z_{22}} = \frac{1}{12} = 0.0833$$
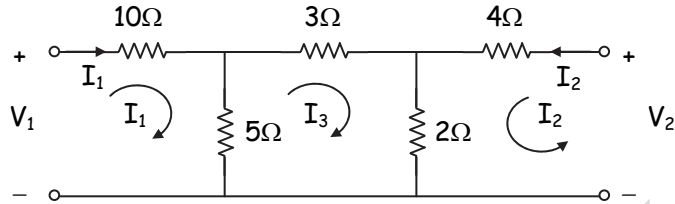
$$\therefore \begin{bmatrix} h'_{11} & h'_{12} \\ h'_{21} & h'_{22} \end{bmatrix} = \begin{bmatrix} 32.66 & 0.333 \\ -2.833 & 0.0833 \end{bmatrix}$$



Apply KVL to I_3

$$-5(I_3 - I_1) - 3I_3 - 2(I_3 + I_2) = 0$$

$$-10I_3 + 5I_1 - 2I_2 = 0$$

$$I_3 = \frac{-5I_1 + 2I_2}{-10}$$

$$I_3 = 0.5 I_1 - 0.2 I_2 \quad \dots(1)$$

Apply KVL to I_1

$$V_1 - 10I_1 - 5(I_1 - I_3) = 0$$

$$V_1 = 10I_1 + 5I_1 - 5(0.5I_1 - 0.2I_2)$$

$$V_1 = 12.5I_1 + I_2$$

$$\therefore Z_{11} = 12.5\Omega \text{ \& } Z_{12} = 1\Omega$$

Apply KVL to I_2

$$V_2 - 4I_2 - 2(I_2 + I_3) = 0$$

$$V_2 = 4I_2 + 2I_2 + 2(0.5I_1 - 0.2I_2)$$

$$V_2 = I_1 + 5.6 I_2$$

$$\therefore Z_{21} = 1\Omega \quad Z_{22} = 5.6 \Omega$$

$$\Delta z = Z_{11} Z_{22} - Z_{12} Z_{21} = 12.5 \times 5.6 - 1 \times 1 = 69$$

Converting Z to h parameters

$$\begin{bmatrix} h''_{11} & h''_{12} \\ h''_{21} & h''_{22} \end{bmatrix} = \begin{bmatrix} 12.32 & 0.178 \\ -0.178 & 0.178 \end{bmatrix}$$

h - parameter of the interconnected network is given by,

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} h''_{11} + h''_{11} & h''_{12} + h''_{12} \\ h''_{21} + h''_{21} & h''_{22} + h''_{22} \end{bmatrix}$$

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 44.98 & 0.511 \\ -3.011 & 0.261 \end{bmatrix}$$

Q.6(a) The characteristic impedance of a high frequency line is 100Ω . [10]
 If its terminated by a load impedance of $100 + j100\Omega$. Using smith chart, find out : (i) VSWR, (ii) Reflection coefficient, (iii) Impedance at $(1/10)^{\text{th}}$ of wave length away from load, (iv) VSWR minimum and VSWR maximum away from the load.

(A) $Z_L = 100 + j100$

$$\bar{Z}_L = \frac{100 + j100}{100} = 1 + j1$$

i) VSWR = 2.6

ii) Reflection coefficient = $0.44 \angle 64^\circ$


iii) Impedance at $\frac{1}{10}^{\text{th}}$ of λ away from load = $2.5 - j0.4$

iv) VSWR minimum = $0.25 \lambda + 0.088 = 0.338 \lambda$

VSWR maximum = $0.25 \lambda - 0.162 \lambda = 0.088 \lambda$

(Smith chart is attached behind)

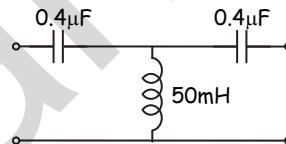Q.6(b) Find the characteristic impedances, cut-off frequency and passband frequency for given network.



[5]

(A) The network is a high pass filter

$$2C = 0.4 \mu\text{F} \quad L = 50 \text{ mH} \quad C = 0.2 \mu\text{F}$$

(i) Characteristic impedance

$$K = \sqrt{\frac{L}{C}} = \sqrt{\frac{50 \times 10^{-3}}{0.2 \times 10^{-6}}} = 500 \Omega$$

(ii) Cut-off frequency

$$f_c = \frac{1}{4\pi\sqrt{LC}} = \frac{1}{4\pi\sqrt{50 \times 10^{-3} \times 0.2 \times 10^{-6}}} = 795.77 \text{ Hz}$$

(iii) Pass band : The pass band is from 795.77 Hz to infinite frequency.

Q.6(c) Explain various types of filters.

[5]

(A) Filters are classified into four categories :

- 1) *Low Pass Filter* : A low-pass filter allows all frequencies up to a certain cut-off frequency to pass through it and attenuates all the other frequencies above the cut-off frequency.
- 2) *High Pass Filter* : A high pass filter attenuates all the frequency below the cut-off frequency and allows all other frequencies above the cut-off frequency to pass through it.

- 3) *Band Pass Filter* : A band pass filter allows a limited band of frequencies to pass through it and attenuates all other frequencies below or above the frequency band.
- 4) *Band Stop Filter* : A band stop filter attenuates a limited band of frequencies but allows all other frequencies to pass through it.

The complete Smith Chart Black Magic Design

