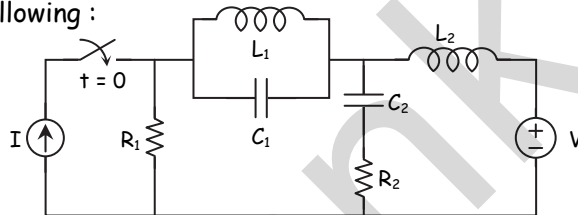



- N.B.:** (1) Question No. 1 is compulsory.  
 (2) Solve any three questions out of remaining.  
 (3) Assume suitable data if required.  
 (4) All questions carry equal marks.

1. (a) Test whether  $P(s) = s^5 + 12s^4 + 45s^3 + 60s^2 + 44s + 48$  is Hurwitz polynomial. [5]

- (b) Draw dual of the following : [5]




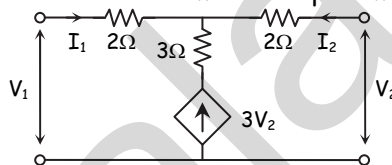- (c) Determine the short circuit admittance parameters of the network shown : [5]




- (d) State and prove final value theorem of Laplace transform. [5]

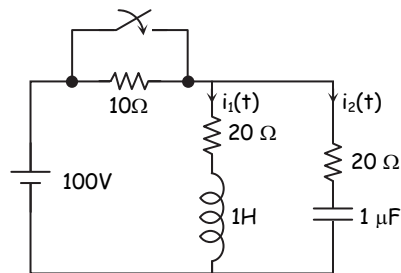2. (a) The network shown in figure, a steady state is reached with the switch open. At  $t = 0$ , the switch is closed. Determine  $V_c(0^-)$ ,  $i_1(0^+)$ ,  $i_2(0^+)$ ,  $\frac{di_1}{dt}(0^+)$  and  $\frac{di_2}{dt}(0^+)$ . [10]




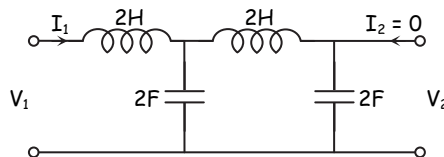- (b) Find the network functions  $\frac{V_1}{I_1}$ ,  $\frac{V_2}{I_1}$ ,  $\frac{V_2}{V_1}$  for the network shown : [5]




(c) In the circuit shown in figure, find  $V_x$ .

[5]

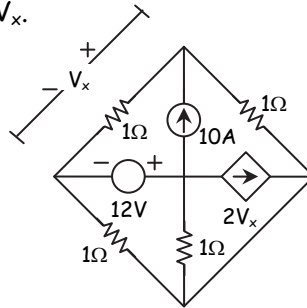

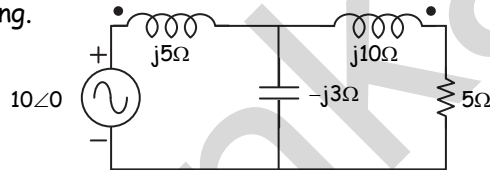3. (a) Find the voltage across  $5\ \Omega$  resistor in the network shown below. If  $K = 0.8$  is coefficient of coupling. [8]




(b) Check the positive real function : [8]


(i)  $F(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}$       (ii)  $F(s) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$

(c) List the types of damping in series R-L-C circuit and mention the condition for each damping. [4]

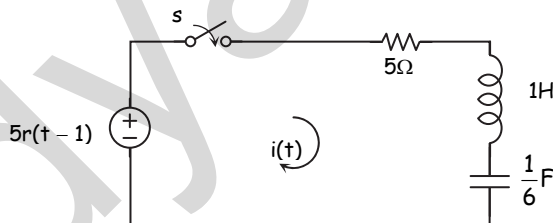
4. (a) For the network shown, determine the current  $i(t)$  when the switch is closed at  $t = 0$  with zero initial conditions. [8]



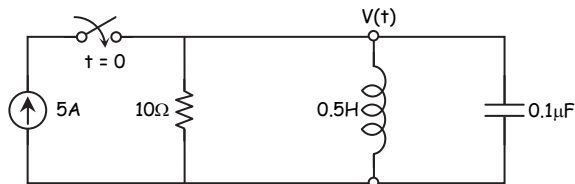(b) In the given network switch is closed at  $t = 0$ . Solve for  $V$ ,  $\frac{dV}{dt}$ ,  $\frac{d^2V}{dt^2}$  at  $t = 0^+$ . [8]



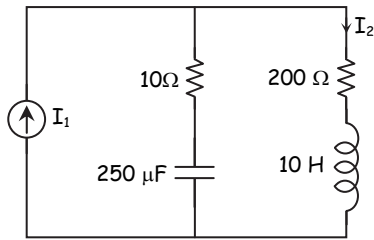(c) Obtain pole-zero plot for  $\frac{I_2}{I_1}$ .




[4]

5. (a) Synthesize the driving point function using Foster - I and Foster - II form :

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$


(b) Obtain hybrid parameter of the inter-connected network.

[10]

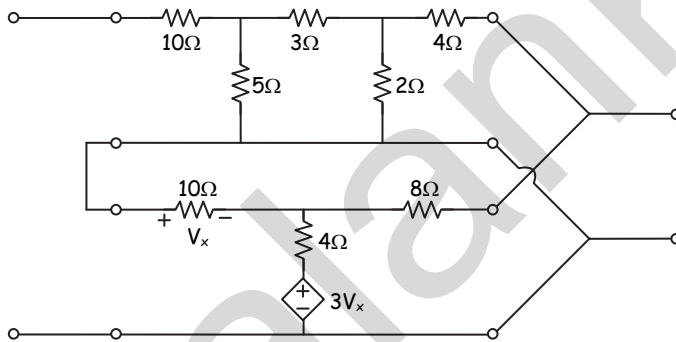


6. (a) For the network shown below, draw a graph of network. Select a tree and obtain :

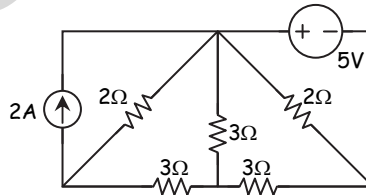- (i) Reduced incidence matrix
- (ii) f-cut set matrix
- (iii) f-tie set matrix



(b) Find  $V_x$  using superposition theorem.

[10]

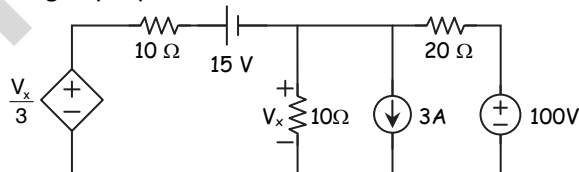

□ □ □ □ □