


S.E. Sem. III [ETRX]
Electrical Network Analysis and Synthesis

Time : 3 Hrs.]

Prelim Paper Solution

[Marks : 80

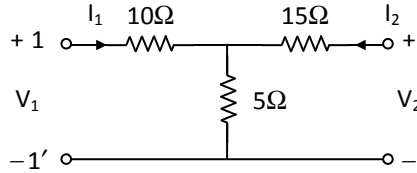Q.1(a) Determine the z-parameters or the network shown in the following figure. [5]




Ans.: Consider z-parameter equations as,

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Consider Case-I $I_2 = 0$

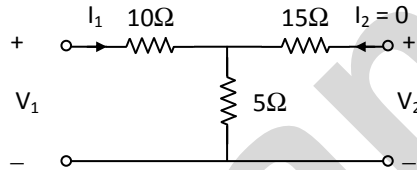


By applying KVL to input side.

$$V_1 - 10I_1 - 5I_1 = 0 \quad \because I_2 = 0$$

$$\therefore V_1 = 15I_1 \quad \therefore Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = 15\Omega$$

$$\text{Also, } V_2 = 5I_1 \quad \therefore Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = 5\Omega$$

Case-II $I_1 = 0$

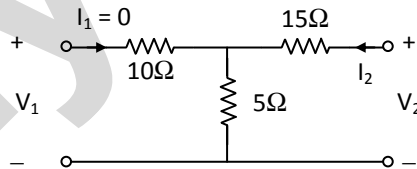

By applying KVL to output side.

$$V_2 - 15I_2 - 5I_2 = 0 \quad \because I_1 = 0$$

$$V_2 = 20I_2 \quad \therefore Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = 20\Omega$$


$$\text{Also } V_1 = 5I_2 \quad \because I_1 = 0 \quad \therefore Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = 5\Omega$$

\therefore Z-parameters are,


$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 15 & 5 \\ 5 & 20 \end{bmatrix}$$

Q.1(b) By mesh analysis determine the current through 2Ω resistor

[5]

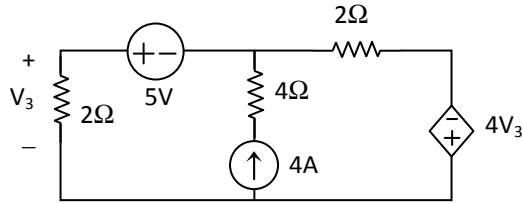

Ans.:

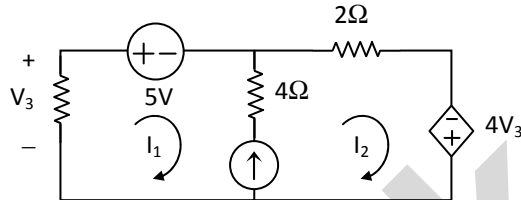

From above circuit

$$I_2 - I_1 = 4 \quad \dots(1)$$

$$V_3 = -2I_1$$

By applying KVL to outer loop,

$$-2I_1 - 5 - 2I_2 + 4V_3 = 0$$

$$\therefore -2I_1 - 5 - 2I_2 - 8I_1 = 0$$

$$-10I_1 - 2I_2 = 5$$

$$\therefore 2I_2 + 10I_1 = -5 \quad \dots(2)$$


By solving equation (1) & (2), we have,

$$I_1 = 2.916 \text{ A} / I_2 = -1.083 \text{ A}$$

\therefore Current through 2Ω is -1.083 A

Q.1(c) Determine the driving point impedance function of the one-port network.

[5]

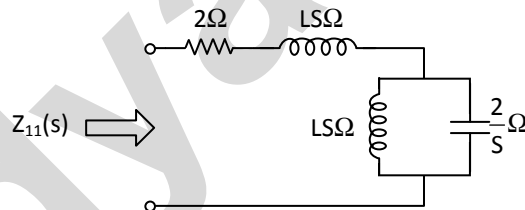

Ans.: $\therefore Z_{11} = (2 + S) + \left[S \parallel \frac{2}{S} \right]$


$$\therefore Z_{11} = 2 + S + \left[\frac{\frac{S \cdot 2}{S}}{\frac{S}{S+2}} \right] = 2 + S + \frac{2S}{S^2 + 2}$$

$$= \frac{2s^2 + 4 + s^3 + 2s + 2s}{s^2 + 2}$$


$$\therefore Z_{11}(s) = \frac{s^3 + 2s^2 + 4s + 4}{s^2 + 2}$$

Q.1(d) Find i , $\frac{di}{dt}$ at $t = 0t$.

[5]

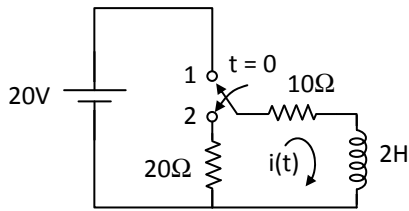

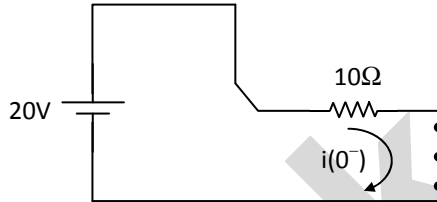Ans.: Step 1: Consider circuit at time $t = 0^-$



$$i(0^-) = \frac{20}{10} = 2A$$


$$i(0^-) = I_0 = 2A$$

At time $t = 0^+$ inductor acts as current source

$$\therefore I(0^-) = I(0^+) = I_0 = 2A$$

$$\therefore I(0^+) = 2A$$

Consider circuit at time $t > 0$.

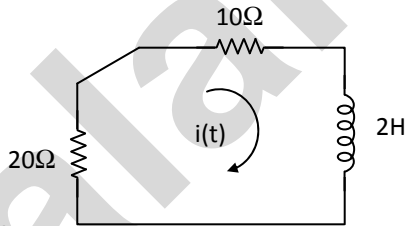

By applying KVL to loop.

$$-20i(t) - 10i(t) - 2 \frac{di(t)}{dt} = 0$$

$$\frac{2di(t)}{dt} = -30i(t)$$


put $t = 0^+$

$$\therefore \frac{di(0^+)}{dt} = \frac{-30}{2} i(0^+) = -30 \text{ A/s}$$


$$\therefore \frac{di(0^-)}{dt} = 30 \text{ A/s}$$

Q.2(a) Find nodal voltages for the given circuit.

[10]

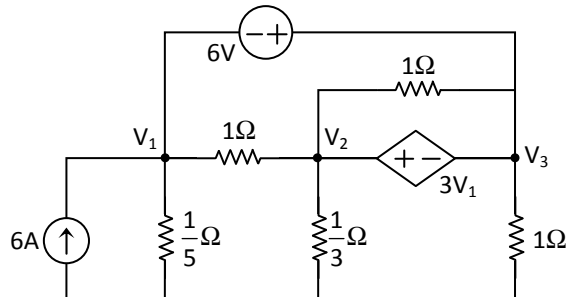

Ans.:

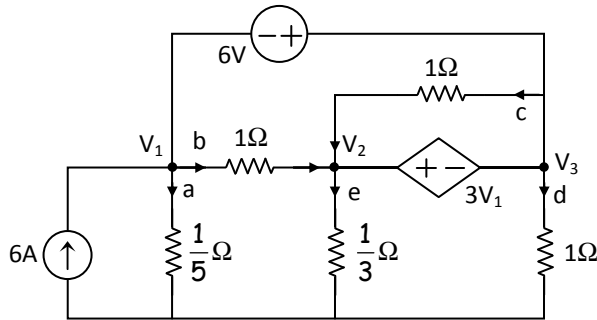

By observing the above circuit,

$$V_1 - V_3 = -6 \quad \dots(1)$$

Also $V_2 - V_3 = 3V_1$

$$\therefore 3V_1 - V_2 + V_3 = 0 \quad \dots(2)$$

By applying KCL at nodes with supernodes,

$$6 - a - b - c - d + c + b - e = 0$$

$$6 - \frac{V_1}{\frac{1}{5}} - \frac{V_3}{1} - \frac{V_2}{\frac{1}{3}} = 0$$

$$-5V_1 - 3V_2 - V_3 = -6$$

$$\therefore 5V_1 + 3V_2 + V_3 = 6 \quad \dots(3)$$

By solving equations (1), (2) & (3) we have,

$$V_1 = -1V, V_2 = 2V, V_3 = 5V$$


$$\therefore V_1 = -1V$$

$$V_2 = 2V$$


$$V_3 = 5V$$

Q.2(b) Determine transmission parameter or the following network.

[5]

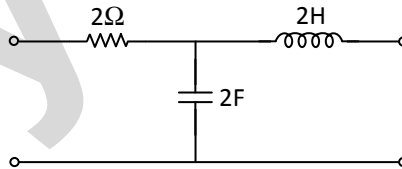

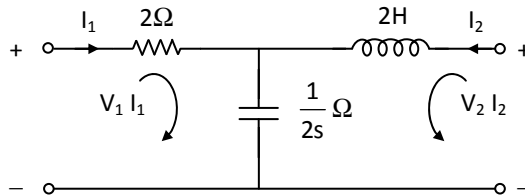Ans.: The Laplace transformed network is given as,



We ABCD parameter equations are

$$V_1 = AV_2 - BI_2 \quad \dots(1)$$

$$I_1 = CV_2 - DI_2 \quad \dots(2)$$

By applying KVL to loop (1) we have,

$$V_1 - 2I_1 - \frac{1}{2S}(I_1 + I_2) = 0$$

$$V_1 = \left(2 + \frac{1}{2S}\right)I_1 + \frac{1}{2S}I_2 \quad \dots(3)$$

By applying KVL to loop (2) we have,

$$V_2 - 2SI_2 - \frac{1}{2S}(I_1 + I_2) = 0$$

$$V_2 = \frac{1}{2S}I_1 + \left(2S + \frac{1}{2S}\right)I_2 \quad \dots(4)$$

$$\therefore I_1 = 2SV_2 - (4S^2 + 1)I_2 \quad \dots(5)$$

Consider equation (3) and put (5) in (3)

$$\therefore V_1 = \frac{(4S+1)}{2S} [2SV_2 - (4S^2 + 1)I_2] + \frac{1}{2S}I_2$$

$$V_1 = (4S+1)V_2 - \frac{(16S^3 + 4S^2 + 4S + 1)}{2S}I_2 + \frac{1}{2S}I_2$$

$$V_1 = (4S+1)V_2 - (8S^2 + 2S + 2)I_2 \quad \dots(6)$$

By comparing equation (6) & (5) with equations (1) + (2)

We have,

$$A = (4S + 1)$$

$$B = 8S^2 + 2S + 2$$

$$C = 2S$$

$$D = 4S^2 + 1$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} (4S+1) & (8S^2 + 2S + 2) \\ 2S & (4S^2 + 1) \end{bmatrix}$$

Q.2(c) Draw oriented graph and find number of trees.


[5]

$$A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

Ans.: To draw oriented graph complete incidence matrix is required.

$$\therefore [Aa] = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \\ 1 & 1 & 0 & 1 & 0 \end{bmatrix}$$

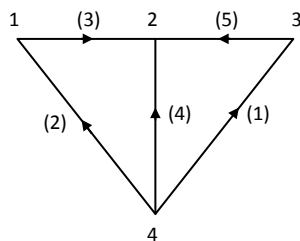For rows as four nodes & five columns as five branches



$$\text{No. of trees} = \text{Det.}\{[A] [A^T]\}$$

$$\text{Consider } \{[A] [A^T]\} = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & 0 & -1 \\ -1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & -1 & 0 \\ 0 & -1 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 2 & -1 & 0 \\ -1 & 3 & -1 \\ 0 & -1 & 2 \end{bmatrix}$$

$$\therefore \text{No. of trees} = \text{Det}\{[A] [A^T]\}$$

$$= \begin{vmatrix} 2 & -1 & 0 \\ -1 & 3 & -1 \\ 0 & -1 & 2 \end{vmatrix}$$


$$= 2 [6 - 1] - (-1) [-2 - 0] + 0 [1 - 0]$$

$$= 10 - 2 = 8$$

$$\therefore \text{Number of trees} = 8$$

Q.3(a) Find the voltage across the 5Ω resistor using mesh analysis.

[10]

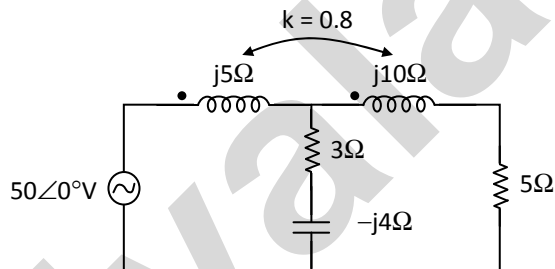

Ans.: The equivalent circuit is given as follows :

Let $k = 0.8$,

\therefore Mutual inductance M is given as


$$X_M = k\sqrt{X_{L_1} X_{L_2}}$$

$$X_M = 0.8\sqrt{5 \times 10}$$

$$X_M = 5.66$$

$$jX_M = j5.66 \Omega$$

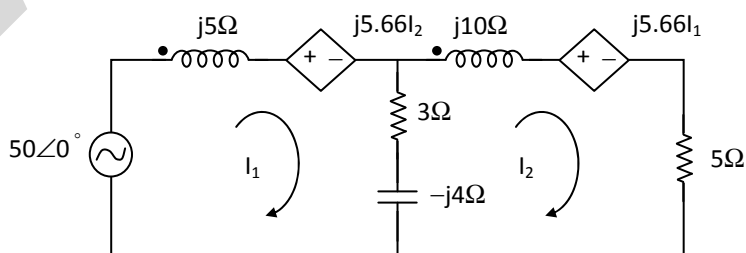Consider current I_1 & I_2 in Loops (1) & (2) respectively,



By applying KVL to mesh L

$$50 - j5I_1 - j5.66I_2 - 3(I_1 - I_2) - (-j4)(I_1 - I_2) = 0$$

$$(3 + j1) I_1 - (3 - j9.66) I_2 = 50 \quad \dots(1)$$

By applying KVL to Loop (2)

$$-j10I_2 - j5.66I_1 - 5I_2 - (-j4)(I_2 - I_1) - 3(I_2 - I_1) = 0$$

$$(3 - j9.66) I_1 - (8 + j6) I_2 = 0 \quad \dots(2)$$

By solving equation (1) & (2) by using Gramer's Rule,

$$I_2 = \frac{\begin{vmatrix} (3 + j) & 50 \angle 0^\circ \\ (3 - j9.66) & 0 \end{vmatrix}}{\begin{vmatrix} (3 + j) & (-3 + j9.66) \\ (3 - j9.66) & -(8 + j6) \end{vmatrix}}$$

$$= \frac{-50(3 - j9.66)}{-(-3 + j)(8 + j6) - [(3 - j9.66)(-3 + j9.66)]}$$

$$= \frac{-150 + j483}{-18 - j26 - 84.315 - j57.96}$$

$$= \frac{-150 + j483}{-102.315 - j83.96}$$

$$= -1.438 - j3.54$$


$$I_2 = 3.82 \angle 67.89$$

$$V_5\Omega = 5I_2 = 5 \times (3.82 \angle 67.89)$$

$$V_5\Omega = 19.1 \angle 67.89^\circ$$

Q.3(b) Determine $V(t)$ for time $t > 0$

[10]

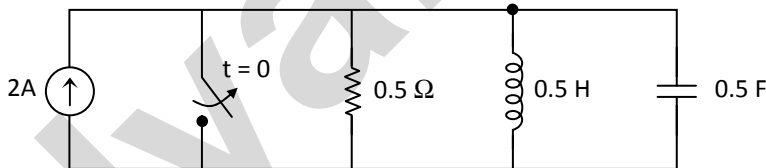


Ans.: To determine $v(t)$ for time $t > 0$

step-I : circuit at time $t = 0^-$ as switch is closed, therefore current source is short circuited.

$$\therefore i_L(0^-) = 0 \text{ \& } V_C(0^-) = 0$$

$$\therefore V(0^-) = 0$$

Step-II : Draw circuit at time $t > 0$.

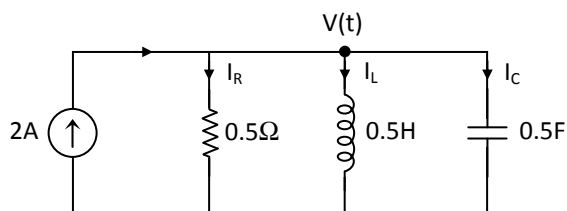

By applying KCL at node v(t)

$$2 = I_R + I_L + I_C$$

$$\therefore I_R + I_L + I_C = 2$$

$$\frac{V(t)}{0.5} + \frac{1}{0.5} \int_0^t v(t) dt + \frac{0.5 dv(t)}{dt} = 2$$

$$\therefore \frac{0.5 dv(t)}{dt} + \frac{V(t)}{0.5} + \frac{1}{0.5} \int_0^t v(t) dt = 2 \quad \dots(1)$$

Diff. w.r.t. 't'

$$\frac{0.5 d^2 v(t)}{dt^2} + \frac{1}{0.5} \frac{dv(t)}{dt} + \frac{1}{0.5} v(t) = 0 \quad \dots(2)$$

put $\frac{d}{dt} = s$

$$\therefore 0.5s^2 + \frac{1}{0.5}s + \frac{1}{0.5} = 0$$

\therefore Roots are $s_1, 2 = -2, -2$

i.e. Roots are real, negative and repeated.

\therefore Therefore solution is given as,

$$V(t) = k_1 e^{s_1 t} + k_2 t e^{s_2 t}$$

$$\therefore V(t) = k_1 e^{-2t} + k_2 t e^{-2t} \quad \dots(3)$$

To find k_1 & k_2 put time $t = 0$

$$V(0) = k_1 + k_2(0)$$

$$\therefore V(0) = 0$$

$$\therefore k_1 = 0$$

\therefore equation (3) becomes,

$$V(t) = k_2 t e^{-2t} \quad \dots(4)$$

Diff. w.r.t. 't'

$$\frac{dv(t)}{dt} = k_2 t e^{-2t} (-2) + k_2 e^{-2t}$$

put $t = 0$

$$\frac{dv(0)}{dt} = +k_2$$

To find $\frac{dv(0)}{dt}$, consider equation (1) put $t = 0$

$$0.5 \frac{dv(0)}{dt} + \frac{0}{0.5} + 0 = 2$$

$$\therefore \frac{dv(0)}{dt} = \frac{2}{0.5} = 4 \text{ v/s}$$


$$\therefore 4 = k_2 \Rightarrow k_2 = 4$$

\therefore equation (4) becomes

$$v(t) = 4t e^{-2t} \quad \therefore t > 0$$

Q.4(a) Determine current in a circuit for time $t \geq 0$.


[10]

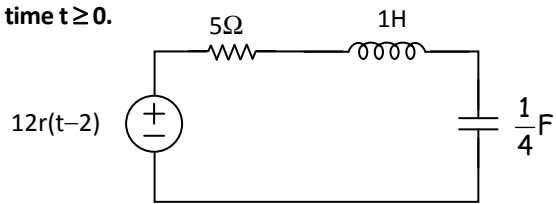

Ans.: As input is delayed and no initial conditions are given

$$\therefore i_L(0^-) = 0A \text{ \& } V_C(0^-) = 0V$$

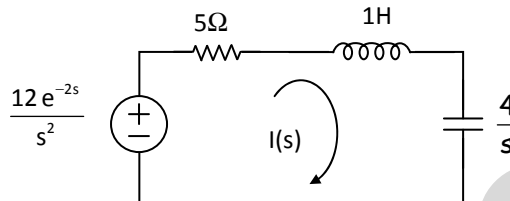Then the Laplace transformed network is given as,



By applying KVL to Loop

$$\frac{12e^{-2s}}{s^2} - 5I(s) - sI(s) - \frac{4}{s}I(s) = 0$$

$$\therefore \left(5 + s + \frac{4}{s}\right)I(s) = \frac{12e^{-2s}}{s^2}$$

$$\therefore I(s) = \frac{12e^{-2s}}{s^2(s^2 + 5s + 4)} \cdot s$$

$$\therefore I(s) = \frac{12e^{-2s}}{s(s+1)(s+4)}$$

Consider,

$$\frac{12}{s(s+1)(s+4)} = \frac{A}{s} + \frac{B}{s+1} + \frac{C}{s+4}$$

$$A|_{s=0} = s \left[\frac{12}{s(s+1)(s+4)} \right] = \frac{12}{(1)(4)} = 3 \quad \therefore A = 3$$

$$B|_{s=-1} = (s+1) \left[\frac{12}{s(s+1)(s+4)} \right] = \frac{12}{(-1)(3)} = -4 \quad \therefore B = -4$$

$$C|_{s=-4} = (s+4) \left[\frac{12}{s(s+1)(s+4)} \right] = \frac{12}{-4(-3)} = 1 \quad \therefore C = 1$$

$$\therefore I(s) = e^{-2s} \left[\frac{3}{s} - \frac{4}{s+1} + \frac{1}{s+4} \right]$$

$$\therefore I(s) = \frac{3e^{-2s}}{s} - \frac{4e^{-2s}}{s+1} + \frac{e^{-2s}}{s+4}$$


By taking I.L.T.

$$i(t) = 3u(t-2) - 4e^{-(t-2)} \cdot u(t-2) + e^{-4(t-2)} u(t-2)$$


$$\therefore i(t) = 3u(t-2) - 4e^{-(t-2)} \cdot u(t-2) + e^{-u(t-2)} u(t-2)$$

Q.4(b) For given graph find
 (i) Incidence matrix
 (ii) tie set matrix
 (iii) f-cut set matrix

[10]

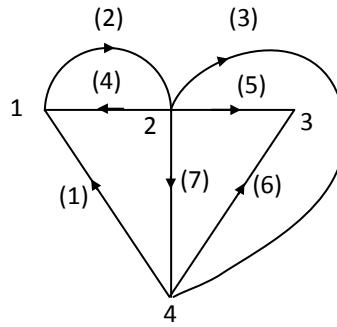

Ans.:

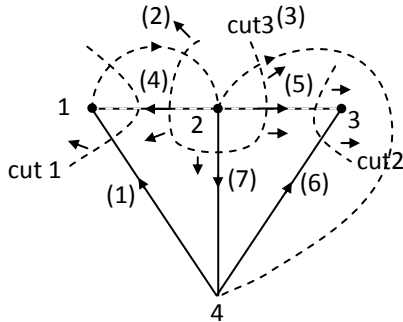

(i) Incidence matrix [A]

To find complete incidence matrix can be written as

$$[A_a] = \begin{matrix} & \text{Branch} & 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ \text{Nodes} & 1 & \begin{bmatrix} -1 & 1 & 0 & -1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 1 & 0 & 1 \\ 0 & 0 & 0 & 0 & -1 & -1 & 0 \\ 1 & 0 & -1 & 0 & 0 & 1 & -1 \end{bmatrix} \end{matrix}$$

$$[A] = \begin{bmatrix} -1 & 1 & 0 & -1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 1 & 0 & 1 \\ 0 & 0 & 0 & 0 & -1 & -1 & 0 \end{bmatrix}$$

(ii) Tieset Matrix [B]

Consider branches 1, 7 & 6 as twing and rest all links forms loops.

Loop1{4, 1, 7}

Loop2{2, 1, 7}

Loop4{5, 6, 7}

Loop5{3, 7}

$$[B] = \begin{matrix} & \text{branch} & 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ \text{Loop} & 1 & \begin{bmatrix} -1 & 0 & 0 & 1 & 0 & 0 & -1 \\ 1 & 1 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 1 & -1 & -1 \\ 0 & 0 & 1 & 0 & 0 & 0 & -1 \end{bmatrix} \end{matrix}$$

- (iii) f-cutset matrix [Q]
 cut1 : {1, 4, 2}
 cut2 : {6, 5}
 cut3 : {7, 2, 3, 4, 5}


	branch	1	2	3	4	5	6	7
f-cut								
[Q] =	1	1	-1	0	1	0	0	0
	2	0	0	0	0	1	1	0
	3	0	-1	1	1	1	0	1

Q.5(a) Realize the foster I and foster II forms of the following impedance function [10]

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$$

Ans.: $Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$

pole-zero plot.

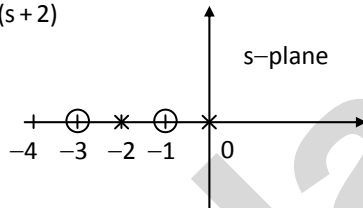

As pole is closer to $j\omega$ axis as pole at origin & zero at -1 , therefore given function is realized by R-C components.

- Foster – I Form :

Let $z(s) = \frac{(s+1)(s+3)}{s(s+2)}$

$$z(s) = \frac{s^2 + 4s + 3}{s^2 + 2s}$$

As Degree of numerator & denominator is same, therefore division is carried out.

$$\begin{array}{r} 1 \\ s^2 + 2s \overline{) s^2 + 4s + 3} \\ \underline{s^2 + 2s} \\ 2s + 3 \end{array}$$

$$\therefore z(s) = 1 + \frac{2s+3}{s^2+2s}$$

$$\therefore z(s) = 1 + \frac{2s+3}{s(s+2)}$$

$$\therefore z(s) = 1 + \frac{k_1}{s} + \frac{k_2}{(s+2)}$$

$$k_1 = s \cdot z(s) \Big|_{s=0} = \frac{(1)(3)}{2} = \frac{3}{2}$$

$$k_2 = (s+2)z(s) \Big|_{s=-2} = \frac{(-2+1)(-2+3)}{-2} = \frac{1}{2}$$

$$\therefore z(s) = 1 + \frac{3/2}{s} + \frac{1/2}{s+2}$$

The first term represents resistor of 1Ω . The second term represent capacitor of $\frac{2}{3}F$


The third term represents the impedance of parallel RC circuit for which,

$$Z_{RC}(s) = \frac{1/Ci}{s + \frac{1}{RiCi}}$$

\therefore By comparing $C = 2F$

$$R = \frac{1}{4}\Omega$$

Foster-I Realization is given as,

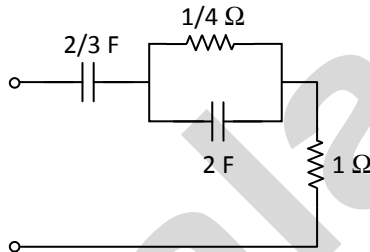

- **Forster – II Form :**

The foster II form is obtained by the partial fraction expansion of admittance function $\frac{Y(s)}{s}$.

$$\text{Let } Y(s) = \frac{1}{z(s)} = \frac{s(s+2)}{(s+1)(s+3)}$$

$$\therefore \frac{Y(s)}{s} = \frac{(s+2)}{(s+1)(s+3)}$$

$$\therefore \frac{Y(s)}{s} = \frac{k_1}{s+1} + \frac{k_2}{s+3}$$

$$\therefore k_1 = (s+1) \cdot \frac{Y(s)}{s} \Big|_{s=-1} = \frac{1}{2}$$

$$k_2 = (s+3) \cdot \frac{Y(s)}{s} \Big|_{s=-3} = \frac{1}{2}$$

$$\therefore \frac{Y(s)}{s} = \frac{1/2}{s+1} + \frac{1/2}{s+3}$$

$$\therefore Y(s) = \frac{\frac{1}{2}s}{s+1} + \frac{\frac{1}{2}}{s+3}$$

These two terms represent the admittance of a series RC circuit. For series RC circuit.

$$Y_{RC}(s) = \frac{\left(\frac{1}{R_i}\right)s}{s + \frac{1}{R_i C_i}}$$


\therefore By direct comparing

$$R_1 = 2\Omega \quad C_1 = \frac{1}{2}F$$


$$R_2 = 2\Omega \quad C_2 = \frac{1}{6}F$$

Foster – II Realization

\therefore

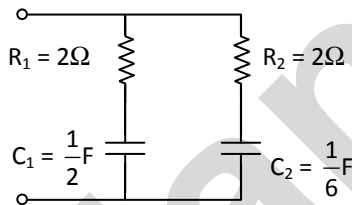


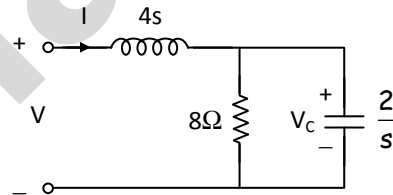Q.5(b) For the given circuit, determine $\frac{V_c}{V}$ & draw the pole-zero plot.



[5]

Ans.: To Determine $\frac{V_c}{V}$

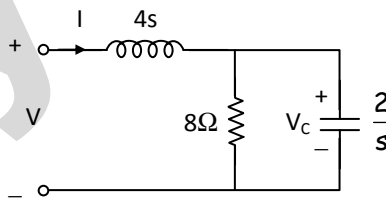

$$\therefore \frac{8 \cdot \frac{2}{s}}{8 + \frac{2}{s}} = \frac{16}{8s+2} = \frac{8}{1+4s}$$

$$\text{Let } V = \left[4s + \frac{8}{1+4s} \right] I$$

$$\therefore V = \left[\frac{4s + 16s^2 + 8}{1+4s} \right] I$$

$$\therefore V = \left[\frac{16s^2 + 4s + 8}{1+4s} \right] I \quad \dots(1)$$

$$\text{Also } V_C = \left[\frac{8}{1+4s} \right] I \quad \dots(2)$$

$$\therefore \frac{V_C}{V} = \frac{[8]1+4s I}{\left[\frac{16s^2 + 4s + 8}{1+4s} \right] I}$$


$$\therefore \frac{V_C}{V} = \frac{8}{16s^2 + 4s + 8}$$

$$\therefore \frac{V_C}{V} = \frac{2}{4s^2 + s + 2}$$

For polezero plot poles are at

$$s_1 = 0.125 \quad \& \quad s_2 = -0.125$$

No zeros

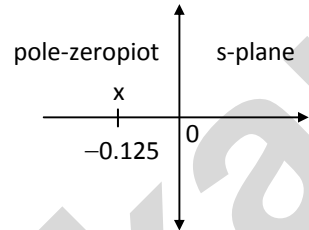

Q.5(c) Check if the following function is a positive real function.

[5]

$$F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$$

Ans.: To check for positive real function

$$F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$$

Step I :

To test N^r & D^r polynomial are Hurwitz or not

$$\therefore F(s) = \frac{N(s)}{D(s)}$$

$$\therefore N(s) = 2s^3 + 2s^2 + 3s + 2 \quad D(s) = s^2 + 1$$

To check for Hurwitz polynomial

Consider, $N(s) = 2s^3 + 2s^2 + 3s + 2$

$$\begin{array}{c|cc} s^3 & 2 & 3 \\ s^2 & 2 & 2 \\ s^1 & 1 & \\ s_0 & 2 & \end{array}$$

All the term's in first column of Routh array are positive, therefore the given polynomial $N(s)$ is Hurwitz.

Consider $D(s) = s^2 + 1$

$$D'(s) = 2s$$

poles at $s^2 = -1$

$$s = \pm j$$

$$\begin{array}{c|cc} s^2 & 1 & 1 \\ s & 2 & \\ s^0 & 1 & \end{array}$$

$\therefore D(s)$ is also Hurwitz polynomial.

Step II :

As poles are on $j\omega$ axis. Hence residue test is carried out.

Let N^r power is greater than D^r power therefore N^r is divided by D^r

$$\frac{(s^2 + 1)2s^3 + 2s^2 + 3s + 2}{(2s + 2)}$$

$$\frac{2s^3 + 2s}{2s^2 + s + 2}$$

$$\frac{2s^2 + 2}{s}$$

$$\therefore F(s) = 2s + 2 + \frac{s}{s^2 + 1}$$

Using partial fraction expansion.

$$F(s) = 2s + 2 + \frac{A_1}{s + j} + \frac{A_2}{s - j}$$

Consider, $\frac{s}{s^2 + 1} = \frac{A_1}{s + j} + \frac{A_2}{s - j}$

$$A_1 \Big|_{s=-j} = (s + j) \cdot \frac{s}{(s + j)(s - j)} \Big|_{s=-j} = \frac{-j}{-j - j} = \frac{1}{2}$$

$$A_1 = \frac{1}{2}$$

$$A_2 = (s - j) \frac{s}{(s + j)(s - j)} \Big|_{s=j} = \frac{j}{j + j} = \frac{1}{2}$$

$$\therefore A_2 = \frac{1}{2}$$

Thus the residues are real and positive.

Step III : Consider even part of $N(s) = m_1 = 2s^2 + 2$

odd part of $N(s) = n_1 = 2s^3 + 3s$

even part of $D(s) = m_2 = s^2 + 1$

odd part of $D(s) = n_2 = 0$

$$\therefore A(w^2) = m_1 \cdot m_2 - n_1 \cdot n_2 = (2s^2 + 2)(s^2 + 1) - (2s^3 + 3s)(0)$$

$$A(w^2) = 2s^4 + 4s^2 + 2$$

put $s = jw$

$$A(w^2) = 2w^4 - 2w^2 + 2$$

$$\therefore A(w^2) \geq 0 \text{ for all } w \geq 0$$

\therefore All three conditions are satisfied, therefore the function is positive real function.

Q.6(a) Check whether the following functions are prf or not :

[10]

$$F(S) = \frac{2S^4 + 7S^3 + 11S^2 + 12S + 4}{S^4 + 5S^3 + 9S^2 + 11S + 6}$$

Ans.: $F(S) = \frac{2S^4 + 7S^3 + 11S^2 + 12S + 4}{S^4 + 5S^3 + 9S^2 + 11S + 6} = \frac{N(S)}{D(S)}$

$N(S) = 2S^4 + 7S^3 + 11S^2 + 12S + 4$	S^4	2	11	4
	S^3	7	12	–
	S^2	$\frac{53}{7}$	4	–
	S^1	$\frac{440}{53}$	–	–
	S^0	4	–	–
$N(S)$ is Hurwitz's polynomial.				
$D(S) = S^4 + 5S^3 + 9S^2 + 11S + 6$	S^4	1	9	6
	S^3	5	11	–
	S^2	$\frac{34}{5}$	6	–
	S^1	$\frac{112}{17}$	–	–
	S^0	6	–	–

$D(S)$ is Hurwitz's polynomial.

Determination of poles,

$$D(S) = 0$$

$$\therefore S^4 + 5S^3 + 9S^2 + 11S + 6 = 0$$

Using synthetic division,

–1	1	5	9	11	6
		–1	–4	–5	–6
	1	4	5	6	0

$$\begin{aligned} \therefore S^4 + 5S^3 + 9S^2 + 11S + 6 &= (S + 1)(S^3 + 4S^2 + 5S + 6) \\ &= (S + 1)(S + 3)(S + 0.5 + j 1.32)(S + 0.5 - j 1.32) \end{aligned}$$

Poles are at $-1, -3, -0.5 - j 1.32$ and $+0.5 - j 1.32$

i.e. roots are complex, real and –ve.

Hence, residuals are not required.

Checking of $A(w)$ function,

where $A(w) = m_1 m_2 - n_1 n_2$

$$m_1 = (2S^4 + 11S^2 + 4) \quad m_2 = (S^4 + 9S^2 + 6)$$

$$n_1 (7S^3 + 12S) \quad n_2 = (5S^3 + 11S)$$

$$\begin{aligned} A(w) &= (2S^4 + 11S^2 + 4)(S^4 + 9S^2 + 6) - (7S^3 + 12S)(5S^3 + 11S) \\ &= (2S^8 + 18S^6 + 12S^4 + 11S^6 + 99S^4 + 66S^2 + 4S^4 + 36S^2 + 24) \\ &\quad - (35S^6 + 77S^4 + 60S^4 + 132S^2) \\ &= 2S^8 - 6S^6 - 22S^4 - 30S^2 + 24 \end{aligned}$$

put $S = jw$

$$\begin{aligned} \therefore A(w) &= 2(jw)^8 - 6(jw)^6 - 22(jw)^4 - 30(jw)^2 + 24 \\ &= 2w^8 + 6w^6 - 22w^4 - 30w^2 + 24 \end{aligned}$$

it is clear that for all values of w , $A(w) \geq 0$


Hence, all conditions are satisfied.

\therefore it is prf.

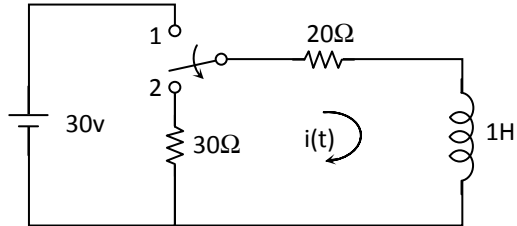
Q.6(b) The network shown in Figure reaches a steady state with switch at position 1. [10]

At $t = 0$, the switch is changed from the position 1 to the position 2, Find the

value of i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$.




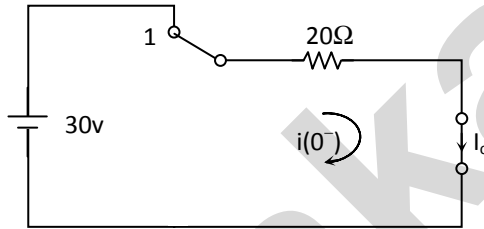Ans.: Draw circuit for $t < 0$ ($t = 0^-$)




$$i_0 = i(0^-) = \frac{30}{20} = 1.5 \text{ Amp}$$

Draw circuit at time $t = 0^+$

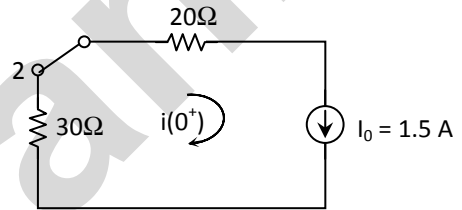

$$i_0 = i(0^+) = 1.5 \text{ Amp}$$

Draw circuit at time, $t \geq 0$

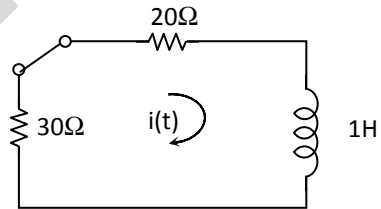

Apply KVL to loop,

$$-30 i(t) - 20 i(t) - 1 \frac{di(t)}{dt} = 0$$

$$\frac{di(t)}{dt} = -50 i(t) \quad \dots (1)$$

put $t = 0^+$

$$\frac{di(0^+)}{dt} = -50 i(0^+) = -50 \times 1.5 = -75 \text{ Amp/sec}$$

Differentiate (1) w.r.t. t

$$\frac{d^2 i(t)}{dt^2} = -50 \frac{di(t)}{dt}$$

put time, $t = 0^+$

$$\frac{d^2 i(0^+)}{dt^2} = -50 \frac{di(0^+)}{dt} = -50 \times (-75) = 3750 \text{ Amp/sec}^2$$

