

Prelim Paper

Time: 3 Hrs.]

Electronic Devices and Circuits I

[Marks : 80


- N.B.:**
- (1) Question No. 1 is compulsory.
 - (2) Attempt any three questions from five questions.
 - (3) Assume Suitable data if required.
 - (4) Figures to the right indicate full marks.

1. Attempt any FIVE questions :


- (a) Explain various types of resistors. [5]
- (b) Why gain of BJT is higher than gain of JFET. [5]
- (c) What is zero temperature drift biasing. [5]
- (d) Consider a BJT has parameters $f_T = 500\text{MHz}$ at $I_C = 1\text{mA}$, $\beta = 100$ and $C_{\mu} = 0.3\text{ pF}$. Calculate bandwidth of f_{β} and capacitance C_{π} of a BJT. [5]
- (e) Write short note on different types of filters. [5]
- (f) Explain the hybrid pi model of BJT. [5]

2. (a) Write short note on DC load line and significance of Q-point [10]
- (b) A full wave rectifier using a center tapped transformer with two diodes gives output voltage of 250 V to a resistive load, the current being $75 \pm 25\text{ mA}$. If the ripple factor is 0.001, calculate the specification of the devices and components required if the filter used are L section LC filter. [10]

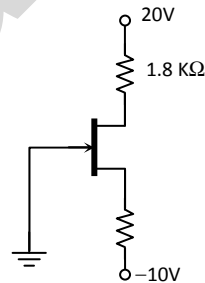3. (a) Obtain expression for gain bandwidth product. [10]
- (b) Determine I_{DQ} , V_{GSQ} , V_{DSQ} if $I_{DSS} = 9\text{ mA}$ and $V_p = -3\text{V}$ for the circuit given in Figure. [10]




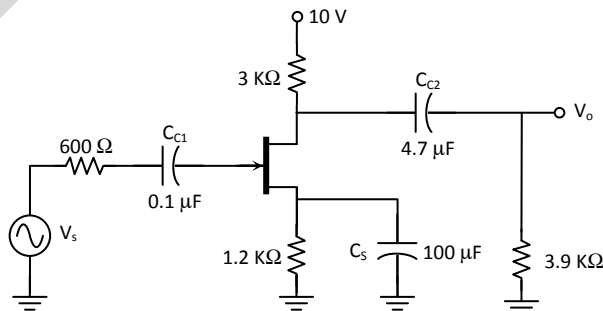4. (a) Design single stage BJT CE Amplifier for the following requirements. [15]
 $A_v \geq 100$, $Z_i \geq 3\text{K}\Omega$, $V_{CC} = 18\text{ V}$
- (b) For above designed circuit calculate A_v , Z_i , and R_o [5]
5. (a) For the circuit using JFET as shown in Figure, if $I_{DSS} = 6\text{ mA}$, $V_p = -6\text{V}$, $r_d = \infty$, $C_{gd} = 4\text{ pF}$, $C_{gs} = 6\text{ pF}$, $C_{ds} = 1\text{ pF}$, determine : higher cutoff frequency. [10]



(b) Find Z_o , Z_i , A_v , A_i for the network given :

[10]

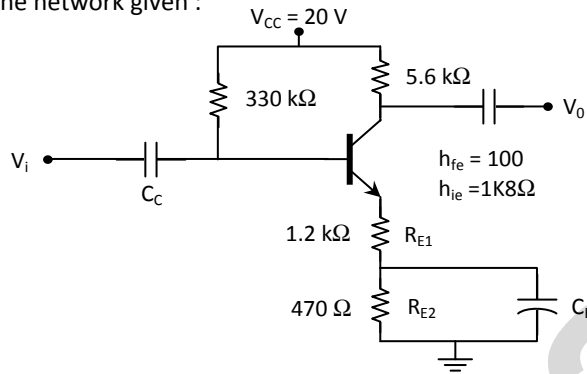

6. Write short notes on (any FOUR) :

[20]

- (a) Millers Theorem
- (b) Stability factors of various biasing techniques of BJT
- (c) Comparison of BJT CE, CB and CC amplifier
- (d) Zener as Regulator
- (e) JFET as VVR.

□ □ □ □ □