

Vidyalankar


F.E. Sem. I
Basic Electrical Engineering (B.E.E.)
List of Formulae

Module -1 D.C. circuits

- $v = IR$ (ohm's law)
- Current divider rule (CDR)
 Applied to parallel circuit only

$$I_1 = \frac{IR_2}{R_1 + R_2}$$


$$I_2 = \frac{IR_1}{R_1 + R_2}$$

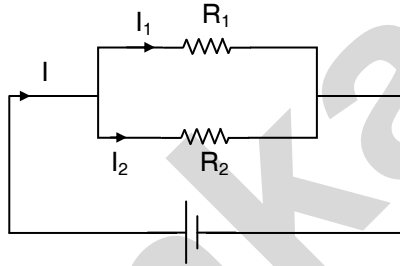


- **Voltage divider rule (VDR)**
 Applied to series circuit only

$$V_1 = \frac{VR_1}{R_1 + R_2}$$



$$V_2 = \frac{VR_2}{R_1 + R_2}$$

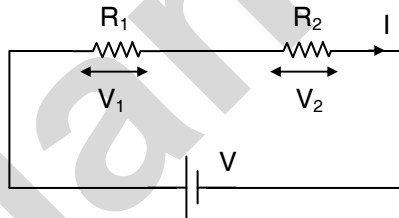

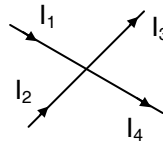- Kirchhoff's current law (KCL)
 Σ Incoming current = Σ outgoing current
 $I_1 + I_2 = I_3 + I_4$



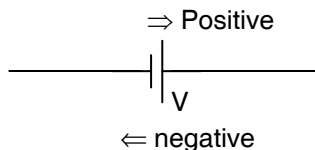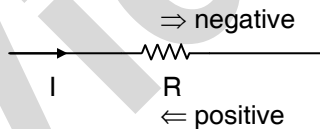- Kirchhoff's voltage law (KVL)
 Over all voltage drop in a loop is equals 0.
 Notations followed.
 Induction of current



- **MESH Analysis**
 mesh is undivided load
 steps:
 (i) Identify meshes
 (ii) Assume clockwise current
 (iii) Apply KVL in each mesh
 (iv) Solve the above equations to get answer.


• **Nodal Analysis**

Node is a junction where current gets split.

Steps

- (i) Identify Nodes
- (ii) At each node assume outgoing current
- (iii) Express current as potential difference upon resistance which can be one of following.


$$I = \frac{N_1 - N_2}{R}$$

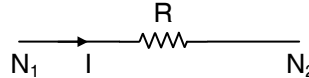


$$I = \frac{N_1 - N_2 + V}{R}$$



$$I = \frac{N_1 - N_2 - V}{R}$$

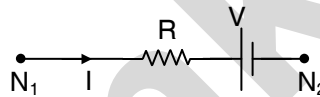

$$I = I'$$

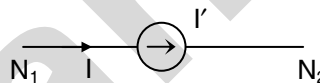

Superposition Theorem

This can be applied wherever we have more than one sources.


Steps :

- 1) Consider one source at a time
- 2) De-merge the sources & replace the sources with its internal resistance if gain. It not green voltage source is replaced with short circuit and current source is replaced with open circuit.
- 3) Find out the current through required resistance using any mechanism like KVL, KCL, mesh or nodal.
- 4) Repeat above steps for all other sources.
- 5) Current through required resistance is algebraic sum of individual current due to individual source. (If current are in same direction then addition else subtraction.)

Thevenin Theorem

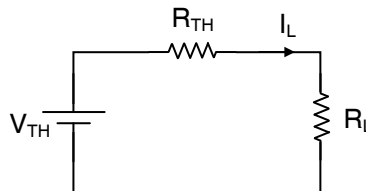- 1) It involves two steps

step 1 $I_L = \frac{V_{TH}}{R_{TH} + R_L}$



Steps :**Step 1**

- 1) De-merge the sources (replace the source with internal resistance if given. If not given voltage source is replaced with short circuit and current source is replaced with open circuit.)
- 2) Replace the substance through which current is required by open circuit name the end points as A and B.
- 3) Find R_{AB} which is R_{TH}

Step 2

V_{TH} same as maximum power the open

Maximum Power

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

STEP to calculate R_{TH} same as in Thevenin refer thevenin.

STEP TO calculate V_{TH} (same in THEVENIN & MAXIMUM power).

- Replace the resistance through which we want current with open circuit. Name the endpoints as A and B.
- Find a path from B to A and across the path add all the voltages as per KVL notation to get the answer which is $V_{AB} = V_{TH}$




NORTON Theorem

Step 1 : find $R_N \Rightarrow$ Step is same as R_{TH}

Step 2 : Find I_N

- Replace the resistance through which we want current with short circuit find the current through the replaced short circuit which is I_N .

Step 3 : $I_L = \frac{I_N R_N}{R_N + R_L}$

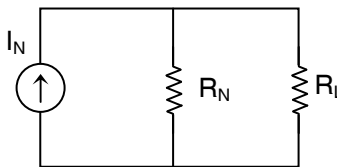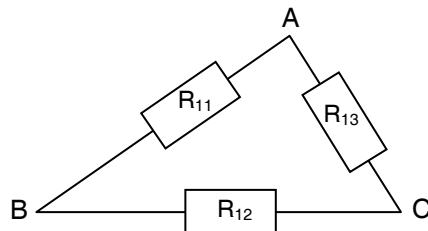
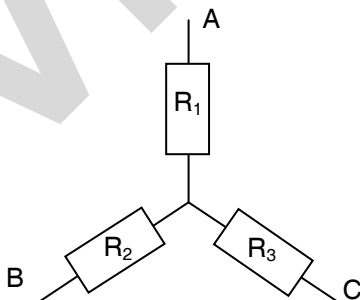
**STAR TO DELTA**

$$R_{11} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{12} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_{13} = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$

DELTA TO STAR

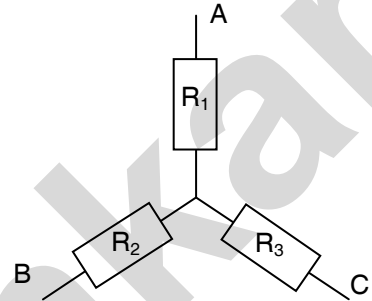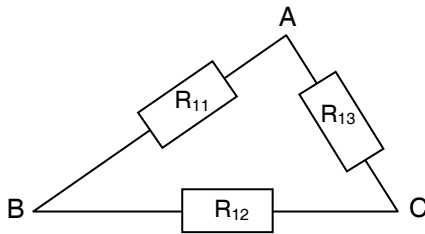


$$R_1 = \frac{R_{11} R_{13}}{R_{11} + R_{12} + R_{13}}$$

$$R_2 = \frac{R_{11} R_{12}}{R_{11} + R_{12} + R_{13}}$$

$$R_3 = \frac{R_{12} R_{13}}{R_{11} + R_{12} + R_{13}}$$

SOURCE Transformation

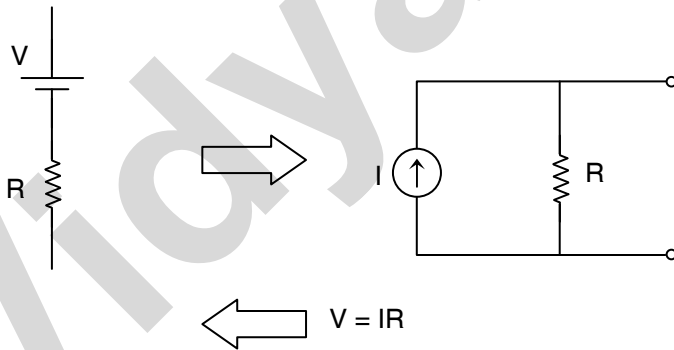

Module -2 A.C. Circuits

- Graph Theory**

$$\text{Average value} = \frac{1}{b-a} \int_a^b f(\theta) d\theta$$

For symmetric signal – half cycle

For asymmetric signal – full cycle

$$\text{RMS Value} = \sqrt{\frac{1}{b-a} \int_a^b f^2(\theta) d\theta}$$


for RMS always full cycle.

- RLC**

For pure R.

→ Voltage and current are in phase.

$$\phi = 0$$

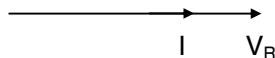


⇒ power factor = $\cos \phi = 1$

For pure L ⇒ $X_L = 2\pi fL$.


⇒ Voltage leads current by 90° , $\phi = 90$

Power factor $\cos \phi = \infty$

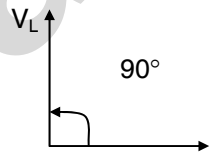

For pure C.

$$X_C = \frac{1}{2\pi fC}$$

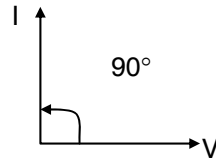


Current leads voltage by 90°




power factor = $\cos 90 = \infty$

RL circuit (also known as choke coil)

$$Z_{eq} = R + j X_L$$





$$i = \frac{V}{Z_{eq}}$$

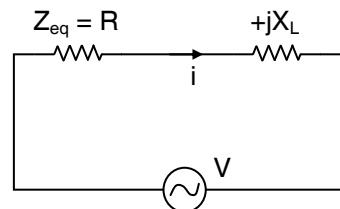

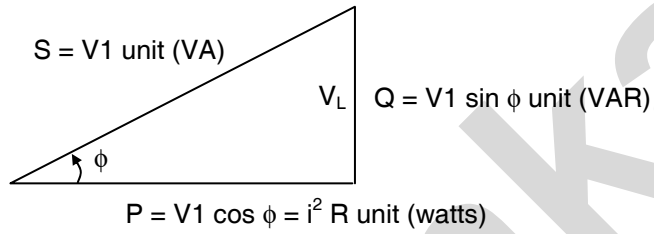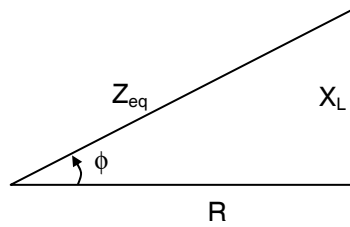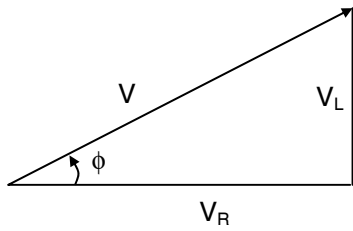


RC Series Circuit

$Z_{eq} = R - jX_C$

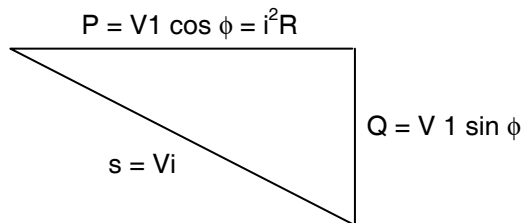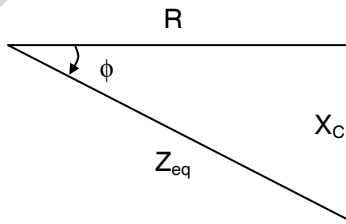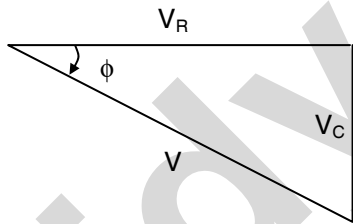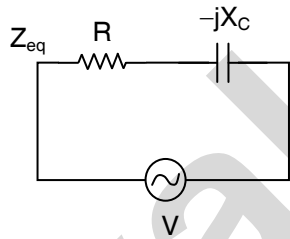




RLC series

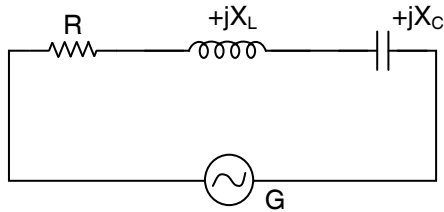

$$Z_{eq} = R + j(X_L - X_C)$$




Two cases rust

(1) $X_L > X_C$

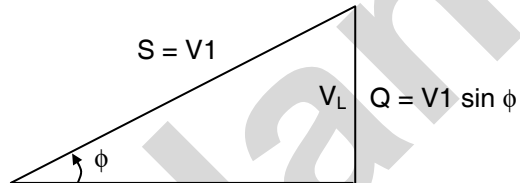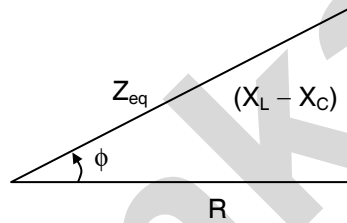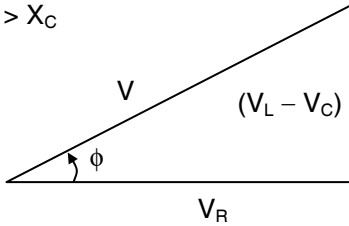

$P = \text{Actual power}$
 $= V1 \cos \phi = i^2 R$

2) $X_C > X_L$

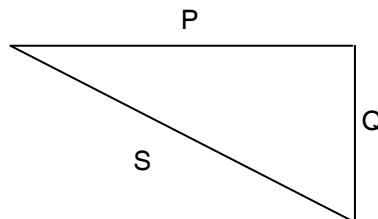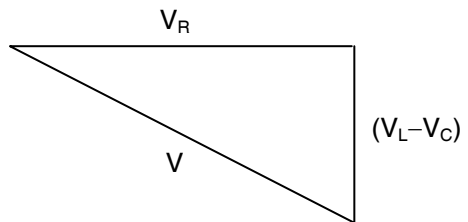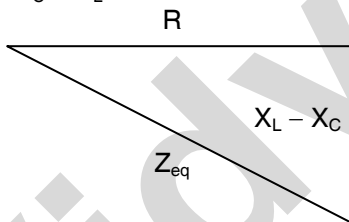

Series resonance

$$Z_{eq} = R$$

$$X_L = X_C$$

$$F_\mu = \frac{1}{2\pi} \sqrt{LC} \text{ Hz}$$

Current maximum
impedance maximum

$$f_2 = \left(f_r + \frac{R}{4\pi L} \right) \text{ Hz}$$

$$f_1 = \left(f_r - \frac{R}{4\pi L} \right) \text{ Hz}$$

$$\begin{aligned} \text{Band width} &= f_2 - f_1 \\ &= \frac{R}{2\pi L} \end{aligned}$$

$$\phi = 0$$

$$\cos \phi = 1$$

Quality factor

$$Q = \frac{1}{2\pi \sqrt{LC}}$$

$$Q = \frac{rf}{BW}$$



Parallel circuit

$$\text{Admittance} \Rightarrow Y_{eq} = \frac{1}{Z_{eq}} \Rightarrow \text{Impedance}$$

$$\text{conductance} \quad G = \frac{1}{R} \Rightarrow \text{resistance}$$

$$\text{Admittance} \Rightarrow B = \frac{1}{X} \Rightarrow \text{inductance or capacitance}$$

For RL
Impedance triangle

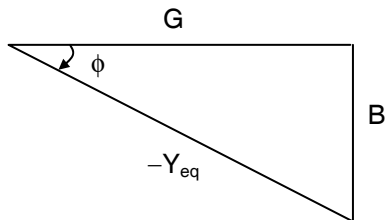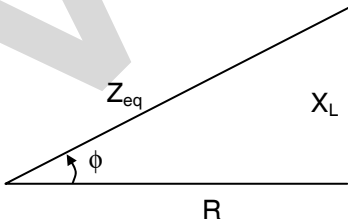

Parallel resonance

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

Impedance is maximum
current is minimum

$$Z_{\text{cail}}^2 = \frac{L}{C}$$

$$Z_{\text{eq}} = \frac{L}{CR}$$

$$\phi = 0$$

$$\cos \phi = 1$$

Module -3 Three phase circuits

For 3 ϕ

$$V_1 = V_m \sin \omega t$$

$$V_2 = V_m \sin (\omega t + 120^\circ)$$

$$V_3 = V_m \sin (\omega t + 240^\circ)$$

For STAR

$$V_L = \text{line voltage}$$

$$I_L = \text{line current}$$

$$V_{\text{Ph}} = \text{Phase voltage}$$

$$I_{\text{ph}} = \text{Phase current}$$

$$V_L = \sqrt{3} V_{\text{ph}}$$

$$I_L = I_{\text{ph}} \quad \text{In both cases}$$

For DELTA

$$V_L = V_{\text{ph}} \quad Z_{\text{ph}} = \frac{V_{\text{ph}}}{I_{\text{ph}}}$$

$$V_L = \sqrt{3} I_{\text{ph}}$$

Power in 3 ϕ

$$P = \text{Active power} = \sqrt{3} V_L I_L \cos \phi$$

$$Q = \text{Reactive power} = \sqrt{3} V_L I_L \sin \phi$$

$$S = \sqrt{3} V_L I_L = \text{Apparent Power.}$$

Power data = 3 Power star

$$Z_{\text{delta}} = 3Z_{\text{star}}$$

For two watt meters

$$W_1 + W_2 = V_L I_L \cos \phi$$

$$W_1 - W_2 = V_L I_L \sin \phi$$

$$\tan \phi = \sqrt{3} \frac{(W_1 - W_2)}{(W_1 + W_2)}$$

Active power = input power

$$\text{Efficiency} = \frac{o/p}{i/p}$$

Module -4 Single phase transformer

$$K = \frac{E_2}{E_1} = \frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2}$$

Transformation ratio

$$\frac{1}{K} = \text{turns ratio}$$

$$E_2 = 4.44 f N_2 \phi_m$$

$$E_1 = 4.44 f N_1 \phi_m$$

$$\begin{aligned} W_u &= I_1^2 R_1 + I_2^2 R_2 \\ &= I_1^2 R_{01} \\ &= I_2^2 R_{02} \end{aligned}$$

R_1 = Primary resistance

R_2 = Secondary resistance

R_1^1 = Primary resistance with respect secondary = $\frac{R_1}{K^2}$

R_2^1 = Secondary resistance with respect Primary = $K^2 R_2$

X_1 = Primary leakage reactance

X_2 = Secondary leakage reactance

X_1^1 = Primary leakage reactance with secondary = $\frac{X_1}{K^2}$

X_2^1 = Secondary leakage reactance with respect to primary = $K^2 X_2$

R_{01} = Total resistance w.r.t. Primary

R_{02} = Total resistance w.r.t. Secondary

X_{01} = Total reactance w.r.t. Primary

X_{02} = Total reactance w.r.t. Secondary

Z_{01} = Total impedance.w.r.t. Primary

Z_{02} = Total impedance.w.r.t. Secondary

$$I_0 = \frac{I_u}{L} + \frac{I_w}{L}$$

No. Load Current Magnetizing Current Coil loss Current

$$I_w = I_0 \cos \phi$$

$$I_u = I_0 \sin \phi$$

$$R_0 = \frac{V_1}{I_w}$$

$$X_0 = \frac{V_1}{I_u}$$

$$\text{KVA} = \frac{E_1 I_1 F_L}{1000} = \frac{E_2 I_2 F_L}{1000}$$

$$\% \text{ Efficiency} = \frac{(x \times \text{KVAFL} \times \text{Pf}) \times 100}{(X \times \text{KVAFL} \times \text{Pf}) W_i + x^2 W_w \text{FL}}$$

$$\eta_{\text{max}} = W_i = W_w$$

$$x = \sqrt{\frac{W_i}{W_w \text{FL}}}$$

$$\% \eta_{\text{max}} = \frac{(x + \text{KVAFL} \times \text{Pf}) \times 100}{(x \times \text{KVAFL} \times \text{Pf}) + 2W_i}$$

Current at any load

$$x = x \text{ current full load}$$

$$\text{KVA}_{\eta_{\text{max}}} = \eta \text{ KVAFL}$$

□ □ □ □ □