

#### Ch. 1: D.C. Circuits:

1. Differentiate between active & passive elements.  
 OR  
 State the 2 types of active elem. (Const. 'V' & Const. 'I')  
 &  
 state the 3 types of passive elem. (R, L & C)
2. State the 3 types of D.C. sources.
3. State the 2 types of A.C. sources.
4. Define R, L, C,  $X_L$  &  $X_C$  alongwith their units.
5. State the Ohm's Law for D.C. circuits.
6. State the " " " A.C. " .
7. State KCL & KVL for D.C. circuits.
8. State the difference between Mesh & Nodal Analysis.
9. What are limitations/disadvantages of Mesh Analysis?
10. What do you mean by linear elements? State their 3 types.
11. State & explain the Superposition, Thevenin's, M.P.T.T. & Norton's Theorems.
12. What is the application of M.P.T.T? (Public Adress System)  
 Why is it not used for electrical machines like transformer?
13. Give/Write the proof of MPTT.
14. State the 2 types of electrical faults. (O.C. & S.C.)
15. Why  $X_L$  &  $X_C$  are not considered in D.C. Circuits?

—X—

#### Ch. 2: A.C. Circuits:

1. Prove that pure L & C do not consume any power.
2. Define Av & RMS values, Form & Peak Factors  
 State their expressions/values for an alternating current.
3. Define cycle, frequency & time period.
4. For an A.C., prove that RMS Value > A.V. Value.
5. " " " " " Peak Factor > Form Factor
6. Draw labelled V- $\Delta$ , Z- $\Delta$  & P- $\Delta$  for R-L, R-C, R-L-C (with  $X_L > X_C$ )  
 R-L-C (with  $X_C > X_L$ ) & a.c. series resonance circuit.
7. Define p.f. 4 ways. State its significance. State its min. & max. values.

OR

State values of p.f. for pure R, pure L & pure C alongwith nature (i.e. lagging/leading)

8. Draw a neat labelled P- $\Delta$  for R-L/R-C circuit.  
Mark on its sides the names, expressions & practical units of the respective powers.
9. Define Y, G & B alongwith their mathematical expressions.
10. Sketch the graphs of  $R$  v/s  $f$ ,  $X_L$  v/s  $f$ ,  $X_C$  v/s  $f$ ,  $Z$  v/s  $f$  &  $I$  v/s  $f$
11. Compare between Series & Parallel resonance.
12. Define dynamic impedance parallel resonance circuit
13. Define Q-factor & Bandwidth. State their expressions.

—X—

### Ch. 3: Three Phase Circuits:

1. Advantages of 3- $\phi$  circuits.
2. Compare between 3- $\phi$  Y &  $\Delta$  connections
3. Draw typical phasor dgm's for Y &  $\Delta$  connections
4. State uses/applications of Y &  $\Delta$  connections.
5. Draw a labelled total power  $\Delta$  for 3- $\phi$  system.
6. Advantages of 2 watt-meter method

or

How can we measure power in 3- $\phi$  circuit with 2 wattmeters?

7. Why a single 3- $\phi$  system is more economical than three separate 1- $\phi$  systems? Explain in brief.
8. State the expressions for total power  $P_T$ , total reactive power  $Q_T$ , p.f. in terms of the 2 wattmeter readings  $W_1$  &  $W_2$ .
9. What precautions will you take if one of the two wattmeters say  $W_1$  starts reading -ve?
10. How can you decide the nature of the 3- $\phi$  load from the readings  $W_1$  &  $W_2$  of the 2 wattmeters?

—X—

### Ch. 4: Transformer (Abbreviated as 'Xr')

1. State the principle of a 1- $\phi$  transformer.
2. State features of a 1- $\phi$  Xr.
3. Define ideal & practical Xr
4. State EMF equations.
5. Define turns ratio, voltage ratio & current ratio.
6. Draw phasor dgm's of ideal & practical X<sup>rs</sup> on no load.

7. Draw phasor diagrams of a practical  $X^r$  supplying resistive, inductive & capacitive loads.
8. Define efficiency of a  $X^r$
9. State the condition for max. efficiency & prove.
10. Define % Voltage regulation & state its practical values for inductive & capacitive loads.
11. State the purposes of O.C. & S.C. Tests of a  $X^r$ .
12. State & explain the 2 types of losses in a  $X^r$ .
13. Sketch/develop the equivalent ckt of a  $X^r$  w.r.t. py. & label the same.
14. How the eq. ckt helps in calculating the 4 parameters of the  $X^r$  viz.  $X_0, R_0, X_{01}$  &  $R_{01}$  ?
15. What will happen if we apply D.C. voltage on the py of a  $X^r$  instead of A.C. voltage ?
16. Why  $X^r$  rating is given in kVA & not in kW ?

—X—